

# T41EP::QSE module::Output transformer

Author: Wald 3Z6AEF [12 Aug 2022]


## Constructor's choice

The diagram of the Rev.010 T41EP QSE module shows the T37-6 output transformer. In the BOM table, T1 transformer is described as type 0553-0013-BC-F [\[1\]](#) (footnotes at the end of the page). Why did the designer choose the T37-6, eventually?

As I was ordering items at Digikey anyway, I added a few 0553-0013-BC-F to my cart, just out of curiosity... Let's do experiment! ?
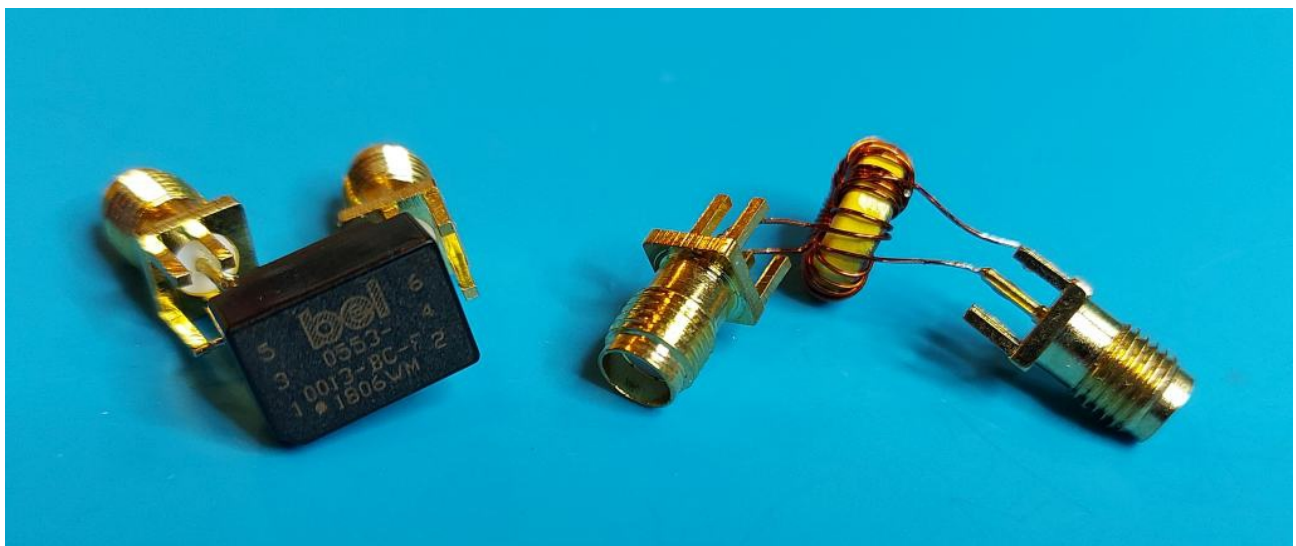
## Transformers



The transformer type 0553-0013-BC-F has a 1:1 ratio (with center tapping) and measured inductance of 1.4 mH (**millihenries**). On the other hand, coil wound with 24T #28 AWG on a T37-6 powder core was measured as only as 1.7uH (**microhenries**).




## Measurement : transmission frequency response


I measured both transformer's transmission frequency response in HF range, using DSA815/TG and nanoVNA-H4.



T37-6 transformer:

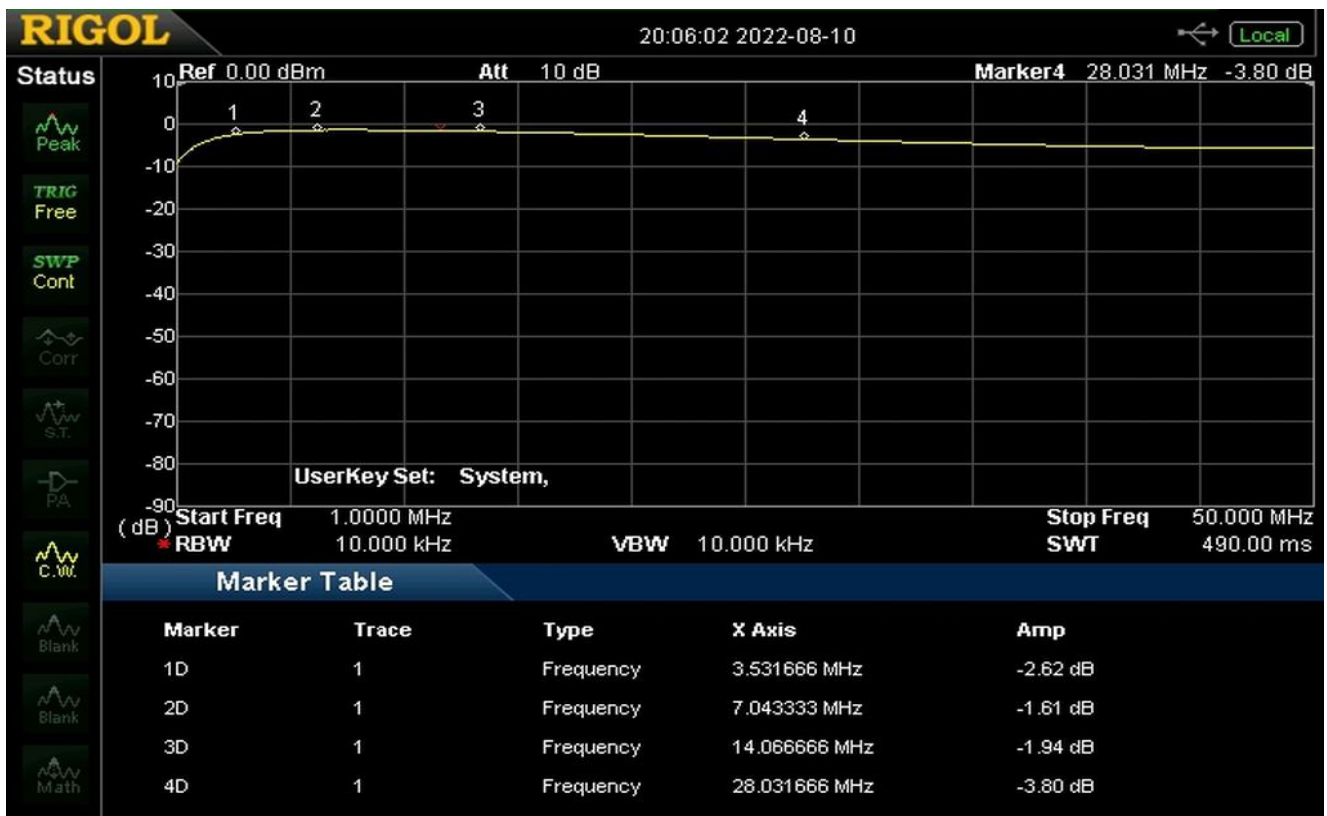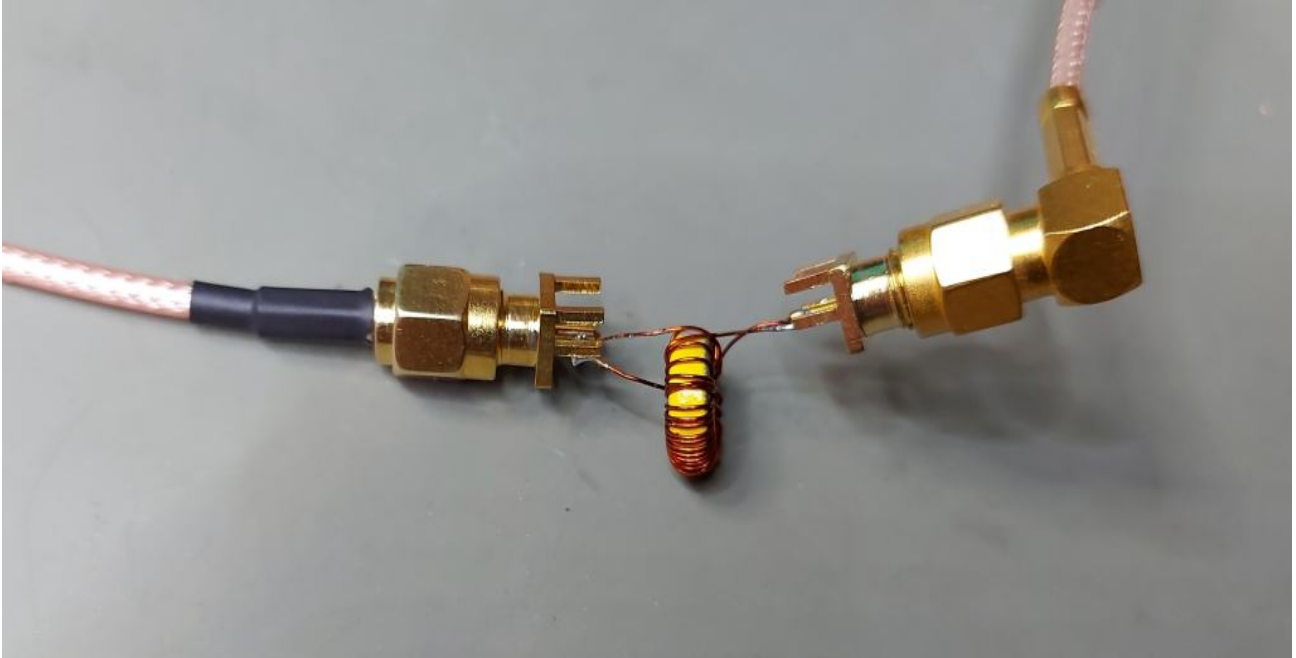

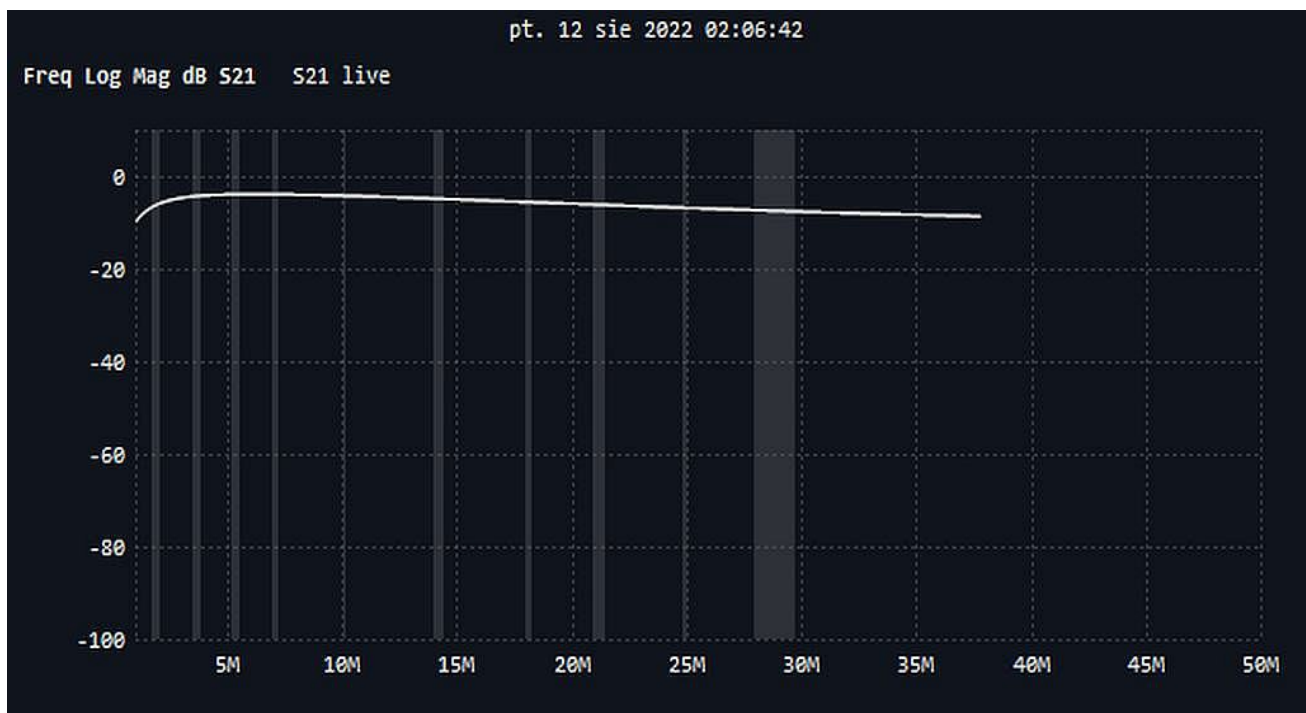

**0553-0013-BC-F transformer:**

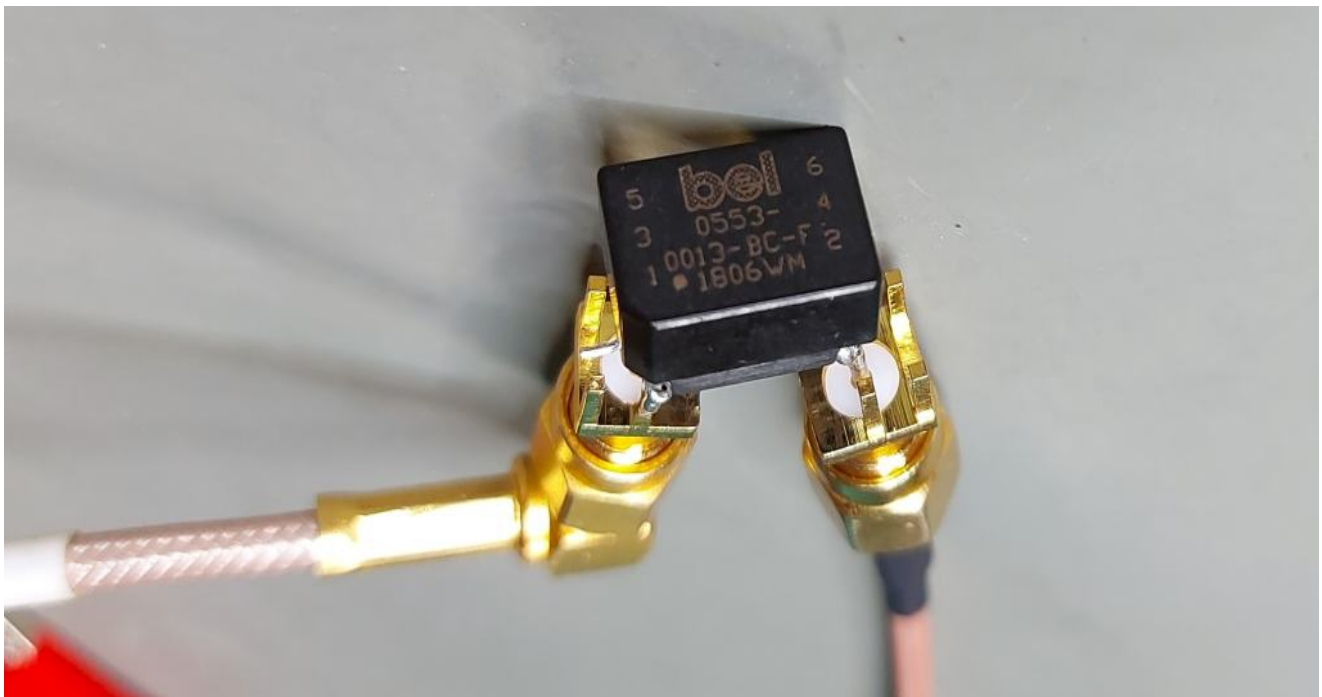

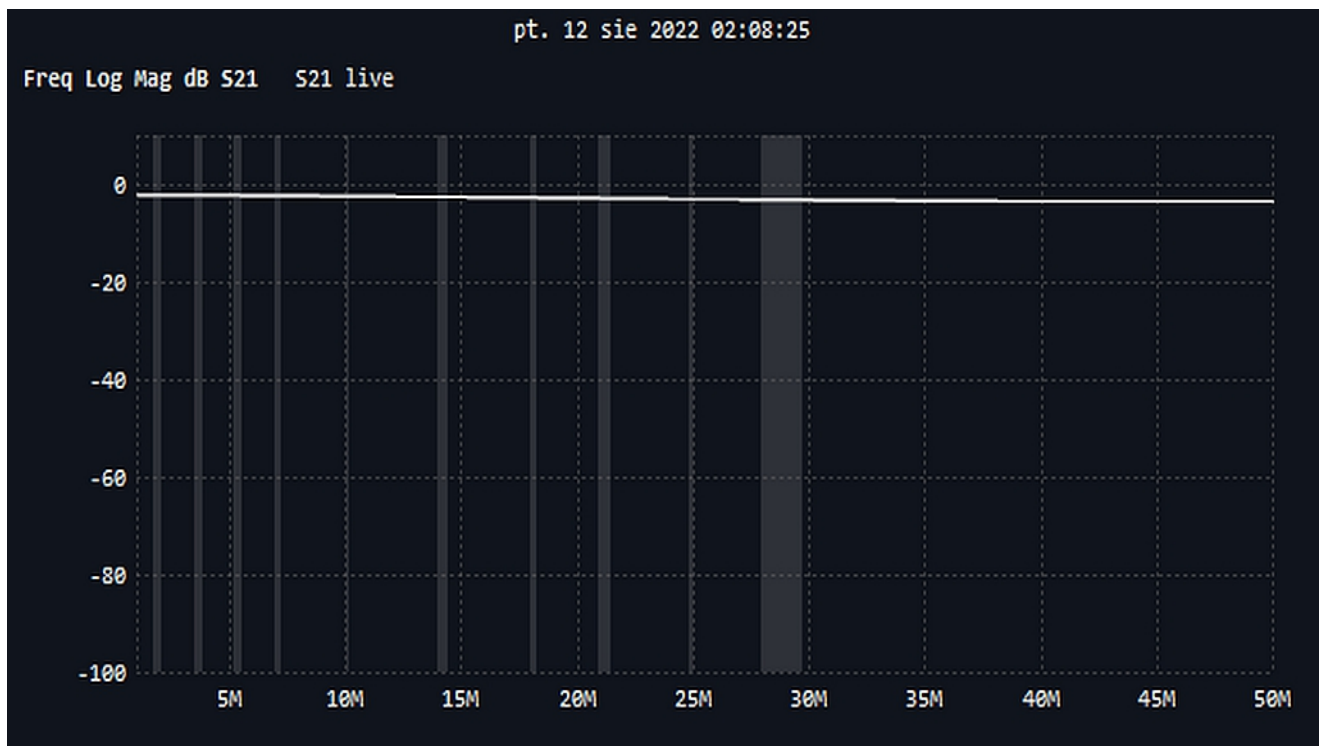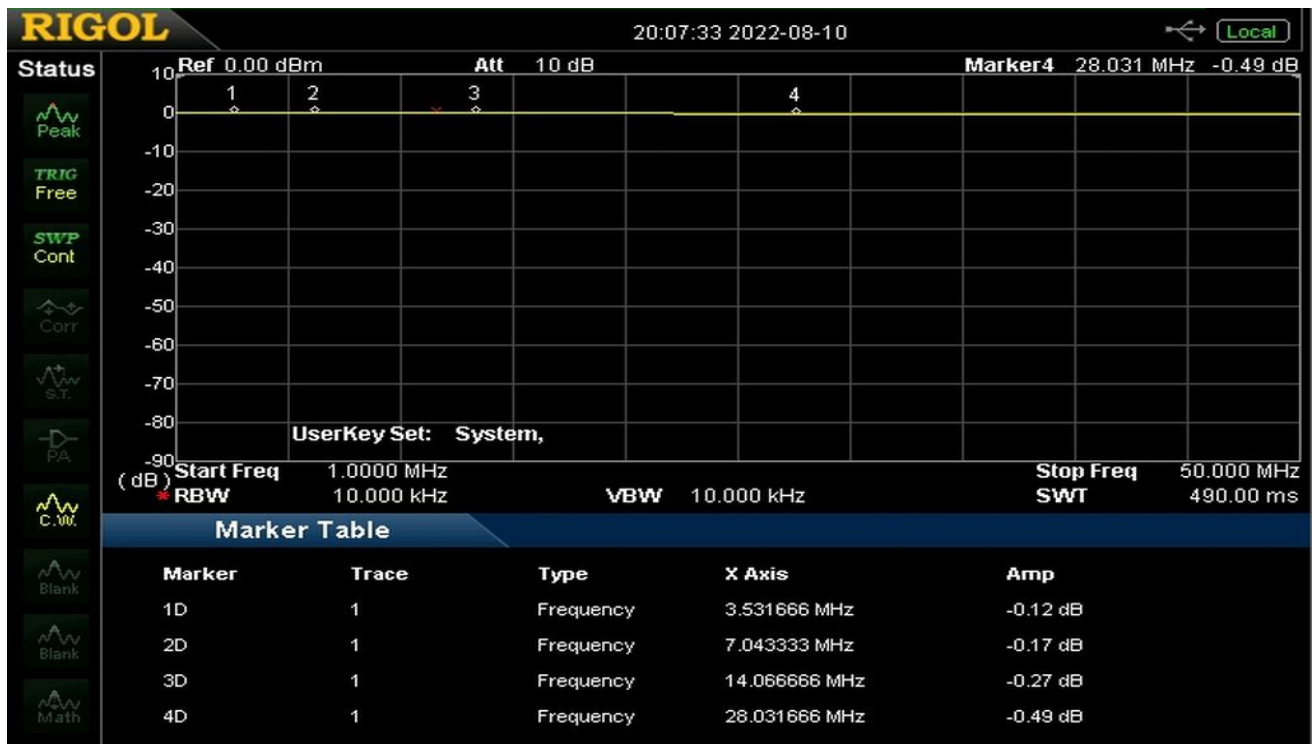


It seems that LAN transformer has better frequency response than T37-6 transformer. But what about reflections?




Measured with nanoVNA-H4, I got

for T37-6 transformer:

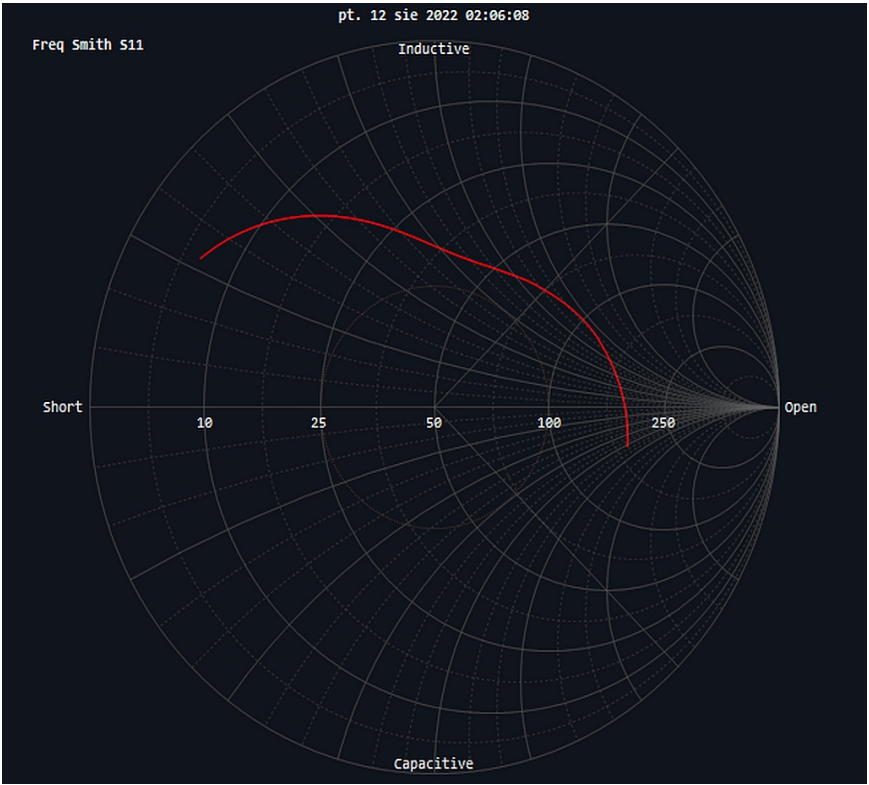


and for 0553-0013-BC-F transformer:

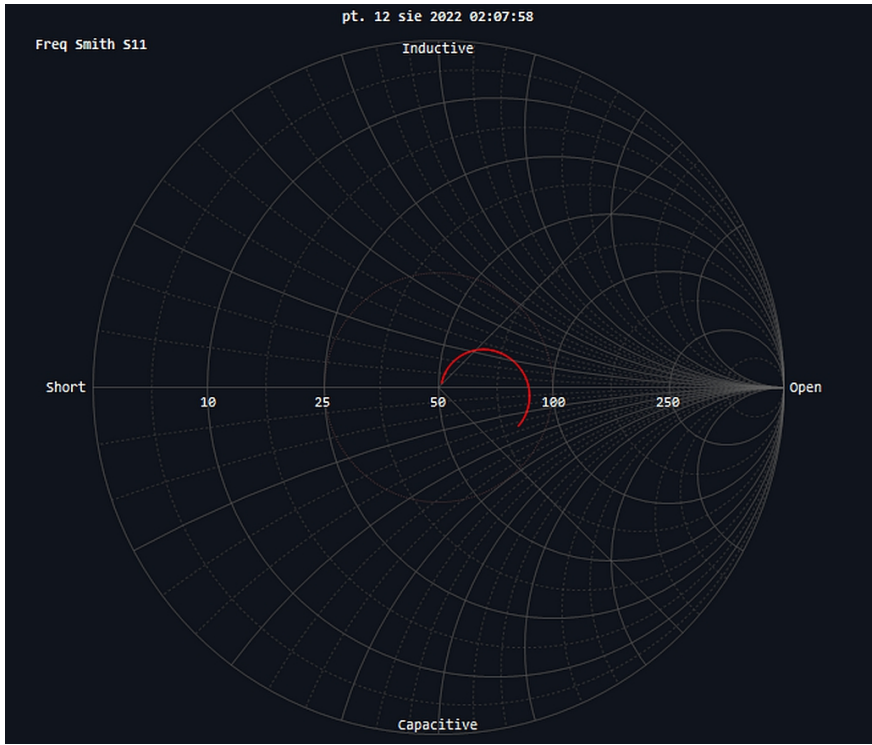

Sooooo...

## Experimenter's choice:

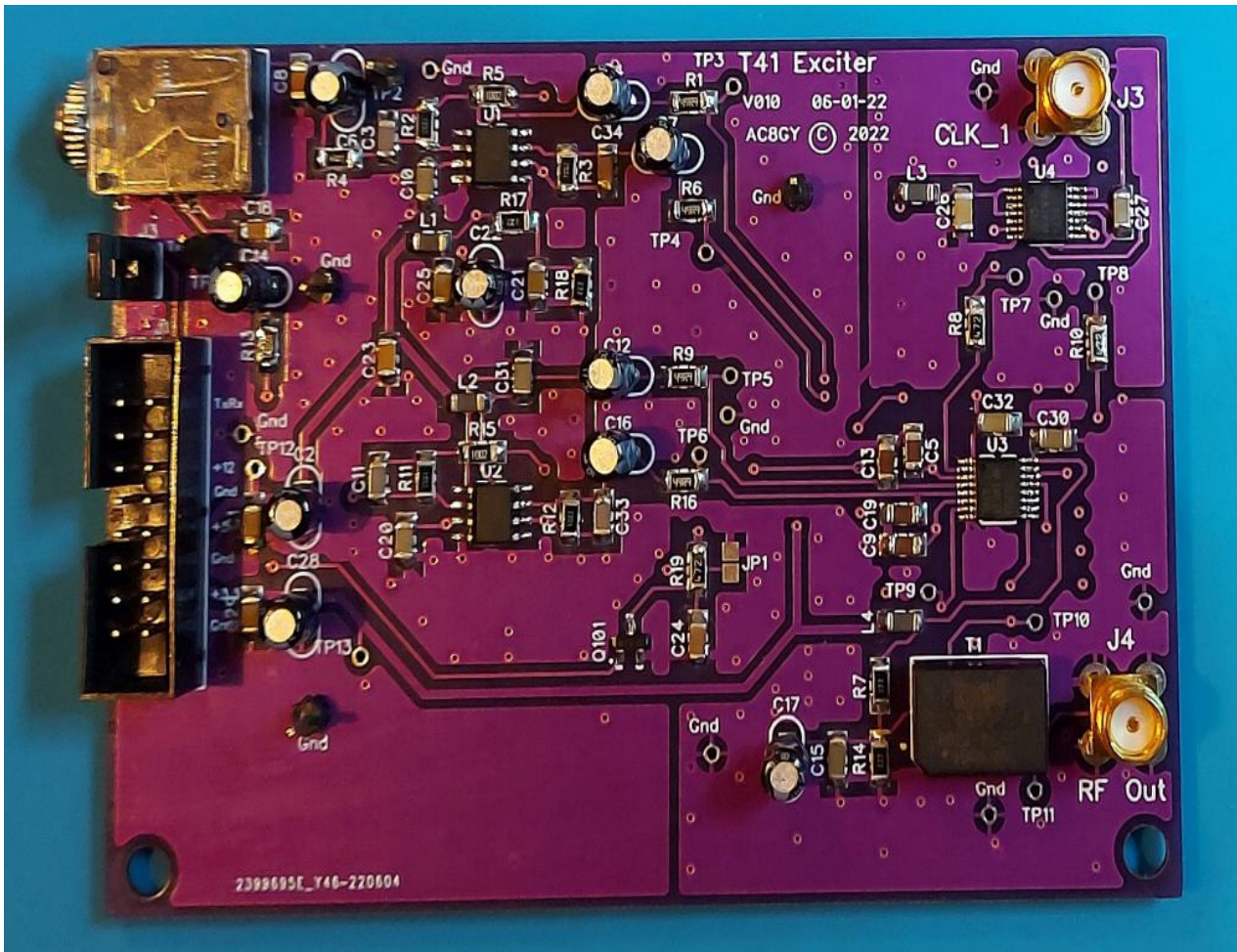

Links and footnotes:

1. 0553-0013-BC-F data sheet:

[https://media.digikey.com/pdf/Data Sheets/Bel Fuse PDFs/0553-0013-BC-F.pdf](https://media.digikey.com/pdf/Data%20Sheets/Bel%20Fuse%20PDFs/0553-0013-BC-F.pdf)