

K9HZ 20W 1-54 MHZ PA
BUILD INSTRUCTIONS for PCB V2.4
June 3, 2024

Operating Data:

Power Requirements: 12-15 VDC at 3A max.

Frequency Range: 1.8MHz – 54Mhz.

Input: 1mw nominal, 50 ohms. Pad provided for higher power input.

Output: 10W or 15W RMS minimum, 20W PEP (see text below), 50 ohms.

Pre-driver: OPA2674ID High Frequency Dual Video Amplifier.

Final Transistor Complement: Push-Pull pair of RD16HHF1-501.

Class of Operation: Normally AB2, but can be any class C-A.

Bias Setting: 250ma per RD16HHF1 for AB2 operation.

PTT: 3-12V positive voltage at J3.

Modes of Operation: AM, CW, SSB, FM.

Inventory and Prework

Before you begin, inventory your parts against the latest BOM to make sure you have everything you need to complete the PA build. The complete BOM is given in Table 1.

Before you start soldering parts onto the PCB, you should also either transcribe the mounting holes for the board onto the heatsink, or make a template of the hole locations from the circuit board on a piece of paper for later use.

Start by examining the board to understand the parts layout in conjunction with the schematic (see Figures 1 and 2). There are a few things you need to decide:

1. Will you be using this PA alone or will you be driving the matching 100W module?
 - a. 20W PA Stand-alone: Then use 2.2K resistors for R6 and R7.
 - b. 20W PA with the 100W Module: Then use 1K resistors for R6 and R7.

The 2.2K feedback resistors will provide up to 15W RMS output. The 1K resistors at these positions will keep the amp to 10W RMS, which is the maximum power the 100W module can tolerate without inserting a power divider pad.

2. Note that the power input of the PA is 1mw RMS and 5mw PEP. Higher input power levels can be accommodated by adjusting R1, R2, and R3 on the input power PAD. Use an appropriate Pi-type Pad calculator to determine R1, R2, and R3 for higher powers as shown in Figure 3.

Building the PA

With a medium heat soldering iron (30-40W), begin the assembly of the PA board in this order:

3. Place semiconductors except for the RD16HHF1s (Q2, Q3) onto the board first. Note the U1 symbol on the PCB is at the top of the part (pin 1 left, pin 8 right, See Figure 4).
4. Place all chip capacitors and resistors on the board. Use the schematic placement if there are any issues reading the part legends on the PCB. **NOTE that C23 is mis-marked on V2.3 and earlier PCBs as C24 (see Figure 5). Also, actual disc capacitor(s) C24 go(es) across T3 primary terminals at the transformer and should be the last component soldered onto the board (e.g. after T3 is soldered to the board). A discussion of the value for C24 is below. C25 (0.1uF) is a board REV 2.4 addition for better RF impedance.**
5. Place all of chip resistors on the board. Only use R25 if the PTT circuit is above 5V (e.g. Is 12V). Otherwise, leave this component position open.
6. Install L1 on the board; L1 is formed from placing the FT43-101 bead onto a lead cut off from a ¼ or ½ watt leaded resistor. The spot is not marked so use the photo below for placement. See Figure 6 for the proper location.
7. Place the one electrolytic capacitor C22 on the board.
8. Place the two bias pots R20 and R21 (mismarked as R26 & R27 on earlier boards).
9. Wind the three transformers (T1, T2, and T3) and the choke (L2):

a. Winding T1

- i. T1 is 3 turns of #30 wire on a BN43-2402 for the primary, and 6 turns center tapped (so 3T+3T) on the secondary.
- ii. You are provided with 36" of #30 transformer wire that has a 155C breakdown temperature for easy stripping and soldering. This wire is used for winding both T1 and T2.
- iii. For T1, begin by cutting the following lengths of wire from that provided:
 1. Cut three pieces of wire 4" long. One will be used for winding the Primary (3T) of T1 and two will be used for winding the secondary (3T each side of the center tap).
- iv. Strip 3/8" of the insulation from one end each of two wires. Do this by placing a blob of solder on the end of your soldering iron and using it to tin 3/8" of the end of both wires. See Figure 7.
- v. Twist the tinned ends together, solder them, and place the legs through the sides of one of the BN43-2403 cores (see Figure 8).
- vi. Wind two more turns using one leg, and two more turns using the other leg for a total of SIX turns (center tapped at 3 turns each) The secondary should now look like you see in Figure 9.

- vii. Now take the remaining 4" piece of wire (cut above) and wind the primary. Start with about 1 inch of wire sticking out of the OPPOSITE side of the core from the primary. Make sure you have 3 passes through BOTH sides of the core for the primary. The completely wound transformer should look like Figure 10.
- viii. Use the same wire-stripping technique used in step "iv" above to complete stripping and tinning all leads on the transformer. Trim the leads to fit the space allotted for T1 on the circuit board. See Figure 11.
- ix. Before installing, Test to see that there is no continuity between the primary and the secondary with an ohm meter.
- x. Solder the transformer into place paying attention to the center tap on the SECONDARY side of the transformer (see figure 12).

b. Winding T2

- i. Like T1, T2 is 3 turns of #30 wire on a BN43-2402 for the primary, and 6 turns on the secondary. The difference is that T2 DOES NOT have a center-tapped secondary, whereas T1 does.
- ii. For T1, begin by cutting the following lengths of wire from that provided:
 - 1. Cut one piece of #30 transformer wire 4" long. This will be used for winding the Primary (3T) of T2.
 - 2. Cut one piece of #30 transformer wire 6" long. This will be used for winding the secondary (6T) of T2.
- iii. Start with the 4" piece of wire. Leave about a 1" lead and wind three turns (3T) on the core. This is the primary of the transformer. See Figure 13.
- iv. On the other side of the core, leave about a 1" lead and wind six turns (6T) This is the secondary of the transformer. Clearly mark the primary and the secondary. See Figure 14.
- v. Use the wire-stripping technique in building T1 above to complete stripping and tinning all four leads on the transformer. Trim the leads to fit the space allotted for T1 on the circuit board. See Figure 15.
- vi. Before installing, Test to see that there is no continuity between the primary and the secondary with an ohm meter.
- vii. Solder the transformer into place paying attention to the PRIMARY and the SECONDARY sides of the transformer (see figure 16).

c. Winding T3

- i. T3 is 2 Turns of #20 silver-coated/ stranded TFE wire center tapped on the primary (1T+1T), and 3 turns on the secondary of a BN43-3312 core.

- ii. You are provided 24" of #20 silver coated copper stranded TFE wire. Cut the wire into 4 pieces of length as given:
 - 1. One piece that is 6" long. This is for L2.
 - 2. Two pieces that are 3 ½" Long. These are for the T3 Primary.
 - 3. What remains in a piece 11" long. This is for the T3 Secondary.
- iii. Set the 6" long piece aside for winding L2 in the next section.
- iv. Strip 3/8" of insulation from one end of each of the two pieces of wire that are 3 ½" long.
- v. Twist and solder the stripped ends together and solder them as shown in Figure 17.
- vi. Place the legs of the wires soldered together through opposite sides of the core as shown in Figure 18.
- vii. Wind an additional half-turn on each leg through the core to complete the 1T+1T primary (see Figure 19).
- viii. Wind the secondary on the opposite side from the primary. Start with one inch of wire protruding from the core on one side, wind three turns through both sides of the core as shown in figure 20.
- ix. Cut the wires back so that only about 3/8" wire protrudes from the core at each wire end. Strip each of the wires back ¼" as shown in Figure 21.
- x. Solder T3 down to the PCB. You can get it tight to the board by soldering down the primary and then using forceps or a small needle nose pliers to hold the secondary leads in place for soldering. The finished product should look like Figure 22.

d. Winding L2

- i. L2 is 7 turns of #20 silver-coated/ stranded TFE wire on a FT50-43 core. (If you want to use the PA down in the 1-3.5 MHz region, use 10 turns).
- ii. Strip ¼" of insulation from one end of the wire. Start winding from that end of the wire leaving about ¼" of insulated wire and the additional ¼" of stripped wire at the starting end.
- iii. Wind 7 turns (7 paths thru the center of the core).
- iv. You can glue the ends of the wire in place on the core with hot glue if you prefer.
- v. At the finish of the 7 turns, leave ½" of wire, and strip that back ¼". See Figure 23.
- vi. Solder one end of L2 to one of the pads for L2 on the circuit board.
- vii. With a forceps or small needle nose pliers, hold the other end of L2 on the remaining solder pad and solder the wire.

10. Finally, Place J1, J2, J3, J4 connectors. Lift the SMA connectors above the board just slightly prior to soldering so that it does not short the center conductor to the connector shell (see Figure 24).
11. Test the board at this point. With a high impedance ohm meter, you should measure several megohms at the power terminal.

Final Steps

12. Drill and tap your heatsink to match the mounting holes on the corners of the board.
13. Place two or three small flat washers under the each of the four corners of the board such that none of the thru-hole parts (PTT connector, power connector, SMA connectors, and bias pots) touch the heat sink. Use a sheet of paper to test that there is clearance.
14. Use the board and RD16HHF1s to find the best places for holes on the heatsink. Drill and tap.
15. Use 1/8" plastic spacers under the corners of the board so it does not short out of the heat sink.
16. Use some heat transfer goop on the RD16HHF1s and screw them down to the head sink. A little goop goes a long way. Solder the leads in place.
17. MARK "+" and "-" ON THE POWER CONNECTOR with a marker. The "+" side is the furthest from the output SMA connector.
18. Connect a 50 ohm resistor across the input connector, and the output to a dummy load via a watt meter, 12-14VDC to the power connection (**WATCH THE POLARITY!**) through an amp-meter capable of at least 4 amps, PTT (positive polarity) to J3. **DO NOT POWER UP YET.**
19. Adjust R20 to and R21 to **fully CLOCKWISE** (CW) position. Check the wiper resistance to ground to make sure its 1K ohms. This indicates the lowest bias point.
20. Power up the amp. The RD16HHF1s should remain cool.
21. Switch on the PTT (J3:1) on (3V is all that is needed). You should see less than 50 milliamps on the amp meter. Adjust slowly R20 CCW to increase the current draw by 250 milliamps. Then adjust R21 CCW to increase the current draw by an additional 250 milliamps. Release PTT.
22. Connect the input to a source of 1mw or less, switch on the PTT (J3). Check the output. Depending how you selected R6 and R7 in Step #1, you should see a minimum of either 10W or 15W output no matter what frequency you are on between 1-54MHz.
23. The amp is now ready for service!

Other Considerations and Performance Enhancements

24. There is some variation in the mixes of the transformer cores, and that can cause slight variations in the frequency response of the PA. What you may see is less gain at 54Mhz than at 1.8Mhz. C24 (Figure 25) is specifically used to correct this situation and flatten the gain curve with frequency. The best way to select C24 is with a spectrum analyzer

or watt meter, plotting the output of the amplifier with frequency for a fixed input of 1mw over that same frequency range.

25. What has been observed is that a value of C24 between 50pf and 350pf can be used to successfully shape the gain curve. Lower values of C24 tend to make the PA generate more gain in the 54Mhz range, whereas values in the 250-350pf range cause more gain in the 21-35Mhz range. If you plan on using the PA only in the 1.8-30 MHz range, use a value of 150pf-350Pf for C24. If you plan to use the PA in the 3.5-50 Mhz, then use values for C24 in the 0-100pf range, the exact value that gives you the flattest gain with frequency as is shown by your specific data for your PA.
26. Note that some gain shaping can also be done by placing small value capacitors across the PRIMARY of T2. This should be done by experimentation.
27. Note that V2.4 boards have a space for an additional C25 capacitor (not listed on the BOM) right at the center-tap of the T3 primary to ground for better RF control. It has been reported that a 0.1uF chip cap here can improve the RF suppression on the DC line and better power out above 30 MHz. You can experiment with this a bit.

Tables and Figures

Table 1. The Latest BOM for V2.4

Part Number	Mouser Part #	Description	Quantity	Board Designator	K9HZ Semi-KIT
C1206C470K5GAC7800	80-C1206C470K5G	CAP CER 47pf 50V X7R 1206	1	C1	0
C1206C104K5RAC7800	80-C1206C104K5RAC7867	CAP CER 0.1UF 50V X7R 1206	15	C2, C3, C4, C5, C9, C10, C12, C13, C14, C15, C17, C20, C21, C23, C25	0
C1206C103K5RAC	80-C1206C103K5RACTM	CAP CER 0.01UF 50V X7R 1206	4	C7, C8, C16, C19	0
CC1206MRV5V98B105	603-CC126MRV5V98B105	CAP CER 1uF 50V Y5V 1206 20%	1	C18	0
CL31A106KBHNNNE	187-CL31A106KBHNNNE	CAP CER 10 UF 50V X7R 1206	2	C6, C11	0
EEV107M035A9HAA	80-EEV107M035A9HAA	Alum CAP SMD 35V 100uF 20%	1	C22	0
K101J15C0GH5TL2	594-K101J15C0GH5TL2	MLCC - Leaded 100pF 100V 5% COG	3	C24*	0
PCB SMA CONNECTORS	712-CONSUMA001-G	PCB Mount SMA Connectors - Female	2	J1, J2	0
PTT Connection - IDC Pins	571-872242	IDC Pins - 1x2 on 2.54MM centers	1	J3	0
Power Connector	651-1715721	Phoenix Terminal Power Connector	1	J4	0
FB-43-101	KITSANDPARTS dot COM	FB43 Small Bead - Single Pass Small Wire	1	L1	1
FT50-43 Core	KITSANDPARTS dot COM	FT50-43 Small Core w/ 7T #20 TFE wire.	1	L2	1
IRLML9301TRPBF	942-IRLML9301TRPBF	IRLML9301TRPBF	1	Q1	1
CPH3455	863-CPH3455-TL-W	CPH3455	1	Q1*	0
RD16HHF1	VARIOUS	RD16HHF1	2	Q2, Q3	2
MMBT3904-HF	750-MMBT3904-HF	MMBT3904 SOT-23	1	Q4	1
RC1206FR-075R1L	603-RC1206FR-075R1L	SMD 5.1 Ohms 250 mW 1206 1%	2	R10, R11	0
RC1206FR-076R8L	603-RC1206FR-076R8L	SMD 6.8 Ohms 250 mW 1206 1%	1	R1	0
RMCF1206FT100R	708-RMCF1206FT100R	SMD 100 Ohms 250 mW 1206 1%	2	R4, R5	0
CRCW1206680RFKEAC	71-CRCW1206680RFKEAC	SMD 680 Ohms 250 mW 1206 1%	2	R2, R3	0
RMCF1206FT750R	708-RMCF1206FT750R	SMD 750 Ohms 250 mW 1206 1%	2	R12, R13	0
RC1206FR-071KL	603-RC1206FR-071KL	SMD 1000 Ohms 250 mW 1206 1%	11	R6, R7, R8, R9, R14, R15, R16, R17, R18, R19, R23	0
CR1206-FX-2201ELF	652-CR1206FX-2201ELF	SMD 2.2K Ohms 250 mW 1206 1%	2	R6*, R7*	0
WCR1206-10KFA	756-WCR1206-10KFA	SMD 10K Ohms 250 mW 1206 1%	3	R22, R24, R25*	0
3296W-1-102LF	652-3296W-1-102LF	Trim Res 1/4W 1Kohms 10% Vertical Adjust 3296W	2	R20, R21	0
BN-43-2402	KITSANDPARTS dot COM	BN-43-2402 Wind with #30 Transformer Wire	2	T1, T2	2
BN-43-3312	KITSANDPARTS dot COM	BN-43-3312 Wind with #20 PTFE Silver Plated Wire	1	T3	1
OPA2674ID	595-OPA2674ID	OPA2674ID	1	U1	1
L78L09ACUTR	511-L78L09ACU	L78L09ACUTR	1	U2	1
#30 Transformer Wire	Remington Industries (eBay)	#30 Transformer Wire	1 ft	For T1, T2	1
#20 PTFE Silver Plated Wire	eBay	#20 PTFE Coated Silver Plated Wire	1 ft	For T3	1
PCB	K9HZ 20W PA PCB	Custom K9HZ PCB	1	PCB	1
	Search Amazon	Aluminum Heat Heatsink 150mm(L) x69mm(W) x36mm(H) - \$12.99 delivered	1	HEATSINK	0

* = Options/ alternates - See Build Text

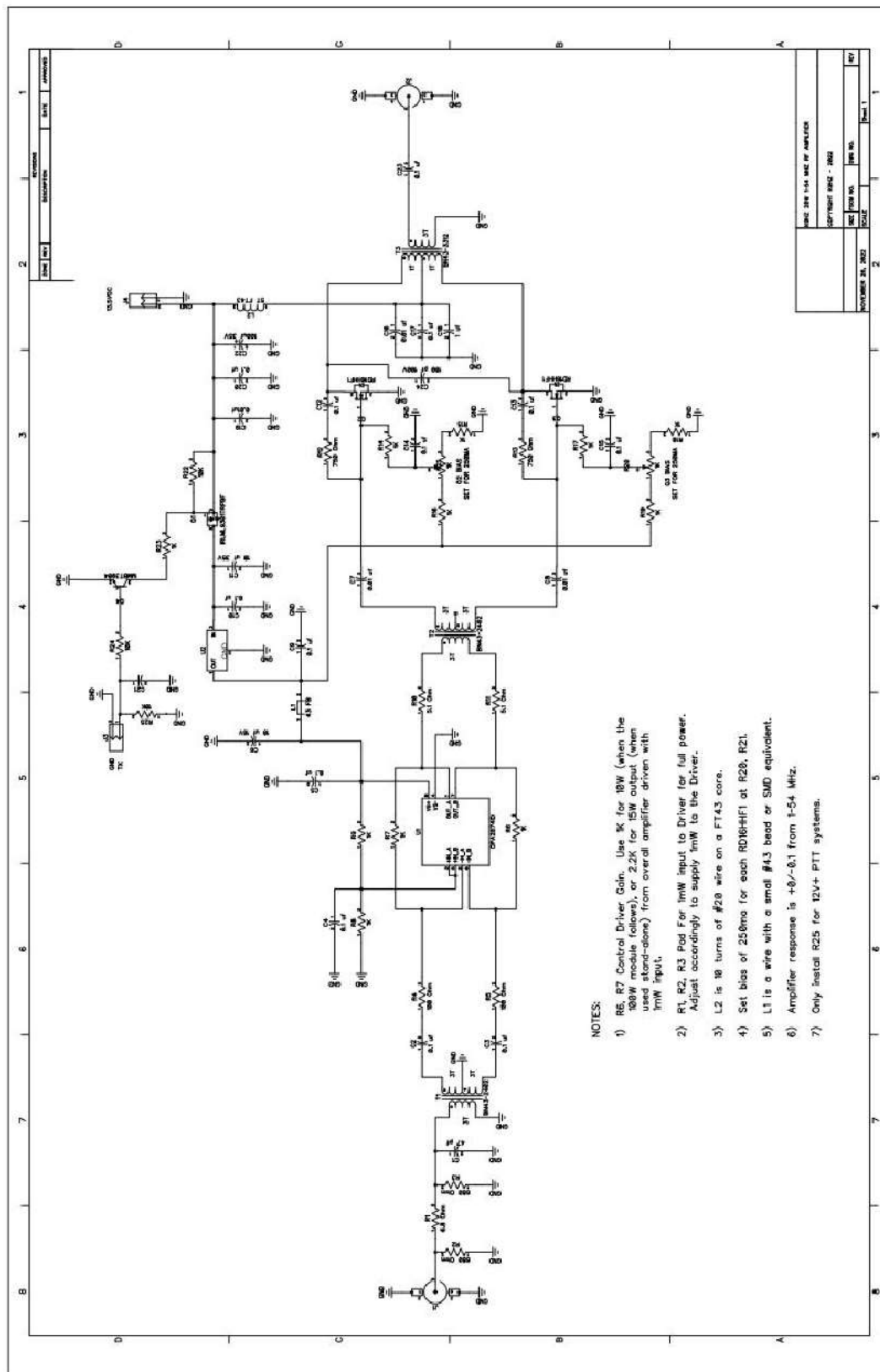


Figure 1. 20W K9HZ 1-54Mhz PA Schematic


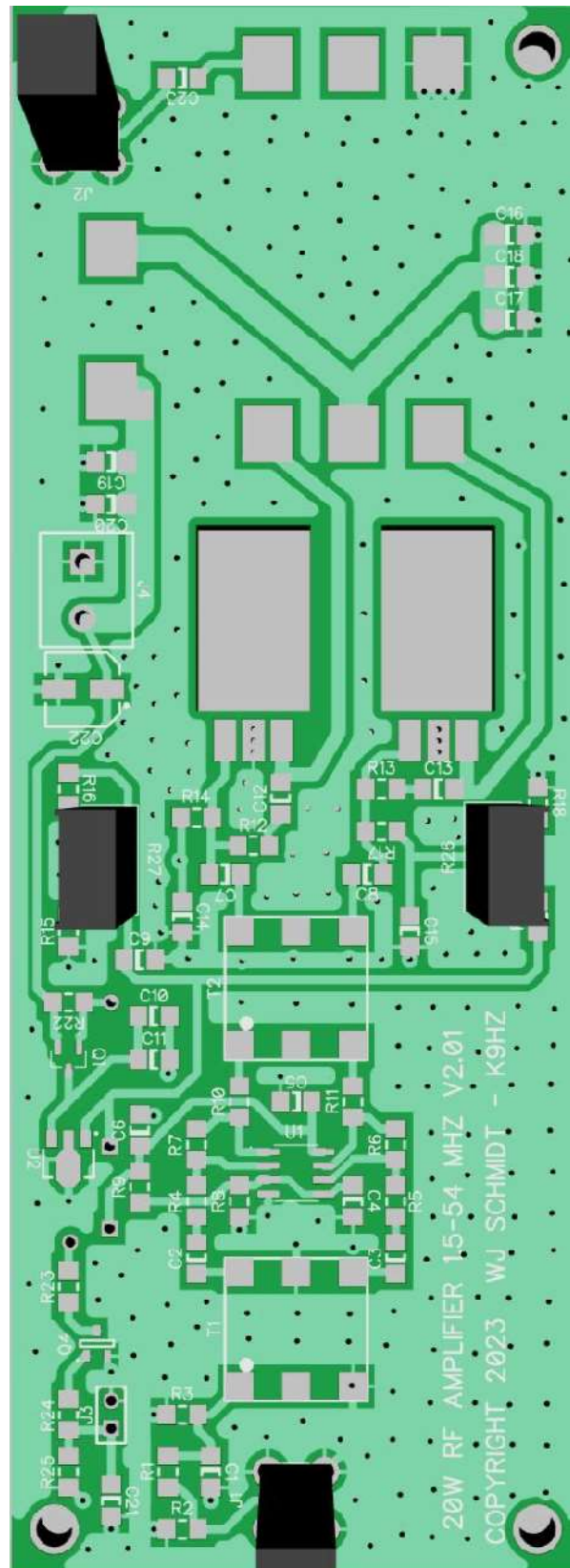


Figure 2. 20W K9HZ 1-54Mhz PCB

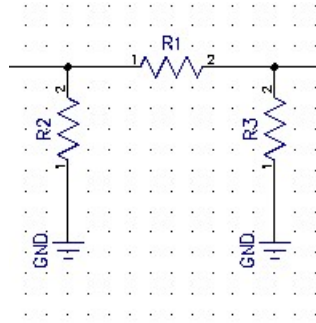

$$Z=50 \text{ Ohms}, \quad K=10^{\left(\frac{\text{Attenuation}}{20\text{db}}\right)}, \quad R1=Z*\frac{(K^2-1)}{2K}, \quad R2=R3=Z*\frac{(K+1)}{(K-1)}$$

Figure 3. Power Divider PAD: PI Attenuator.

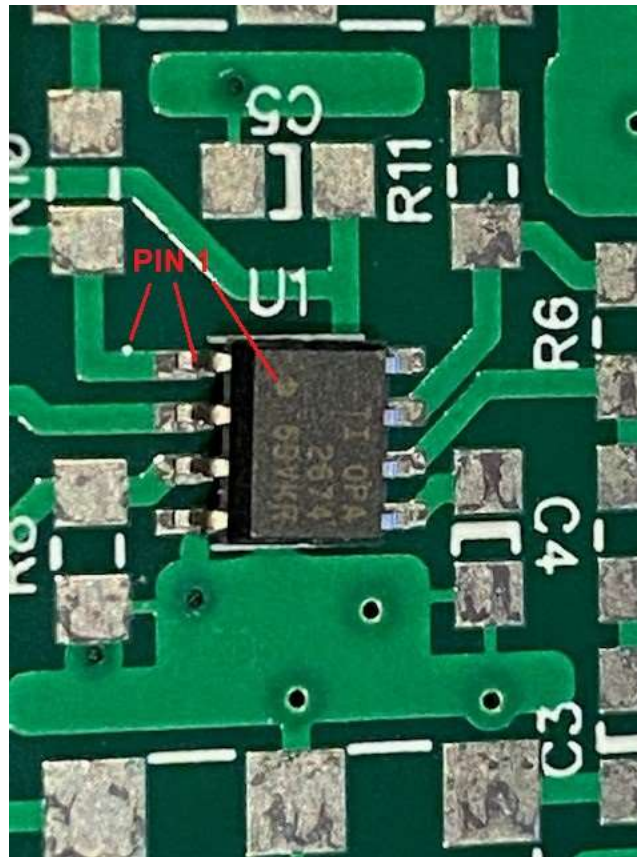


Figure 4. Location of PIN-1 For OPA2674 Part Placement On The PCB

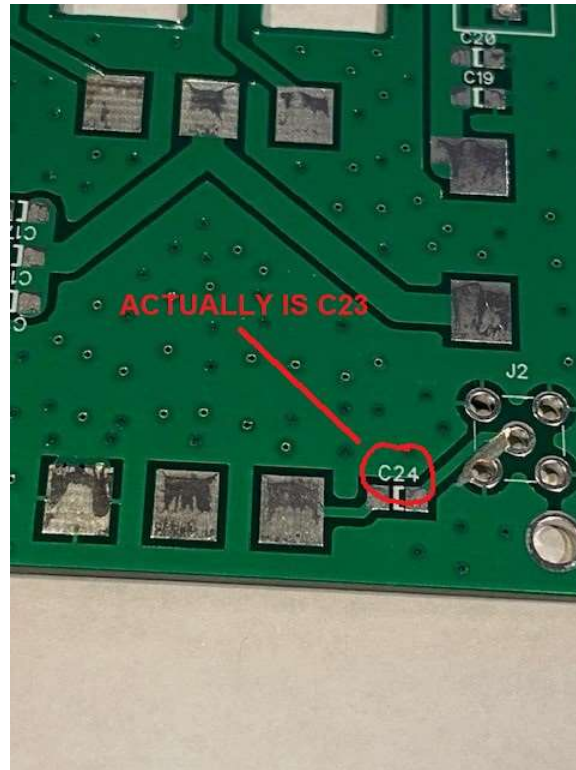


Figure 5. C24 Mislabeled. This Is Actually C23.

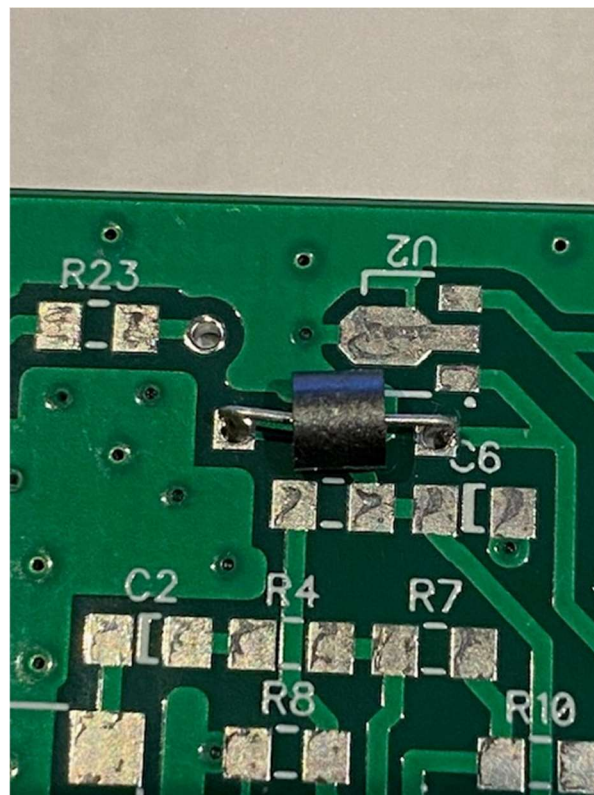


Figure 6. Placement Of L1 – FT43-101 Bead.



Figure 7. Using Solder to Strip Magnet Wire.

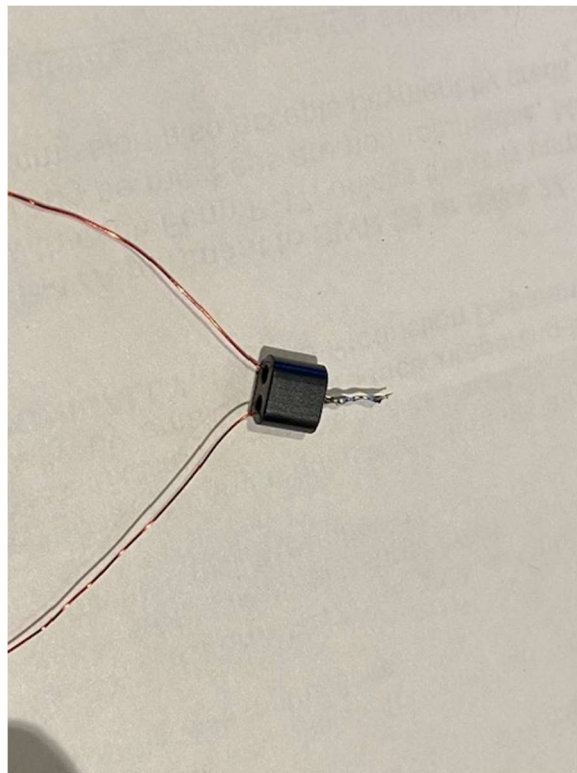


Figure 8. Soldered Legs Forming CT Inserted In B43-2403 Core.

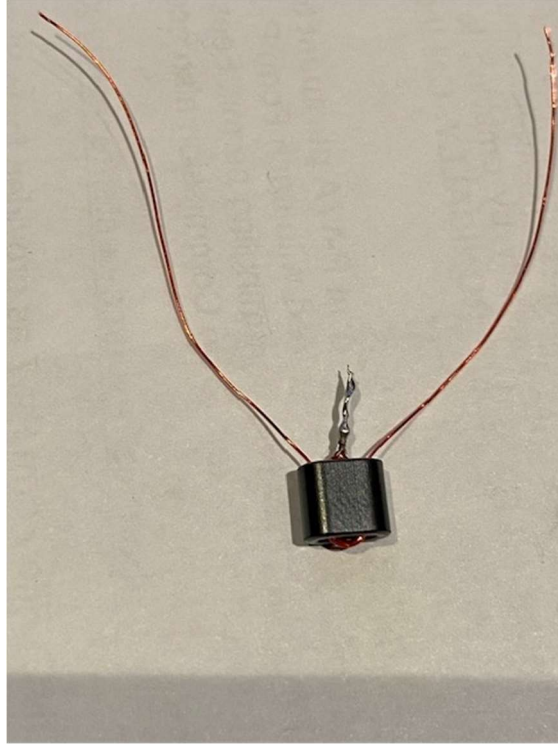


Figure 9. Completed T1 Secondary – 3T + 3T.

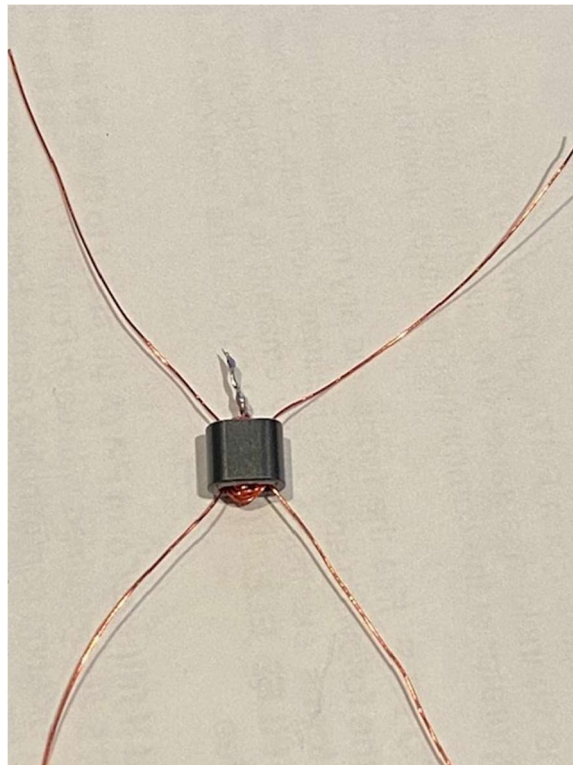


Figure 10. T1 Transformer Windings Completed.

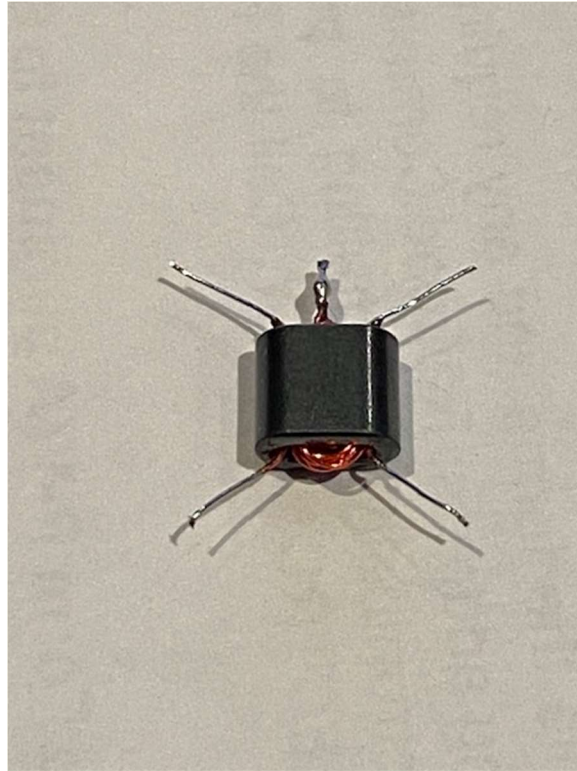


Figure 11. Trimmed T1 Transformer Leads Ready For Soldering On The PCB.

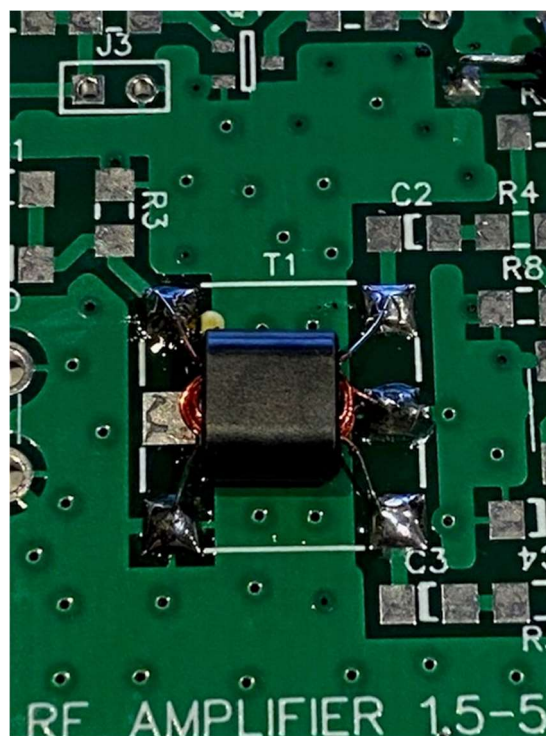


Figure 12. T1 Transformer Soldered In Place On The PCB.

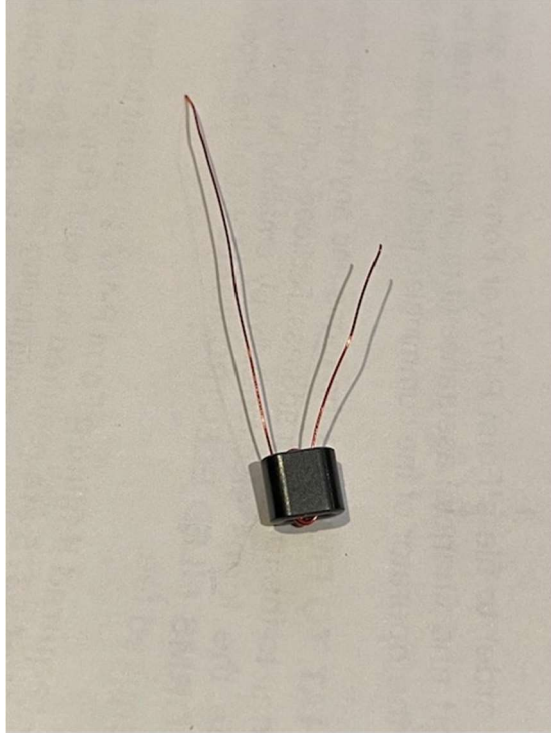


Figure 13. T2 Transformer Primary – 3T of #30 Magnet Wire.

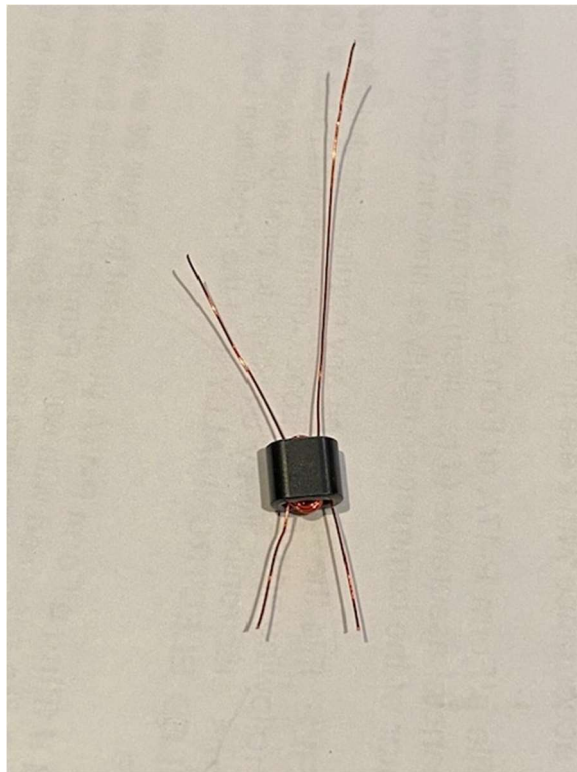


Figure 14. T2 Transformer Secondary Completed – 6T of #30 Magnet Wire.

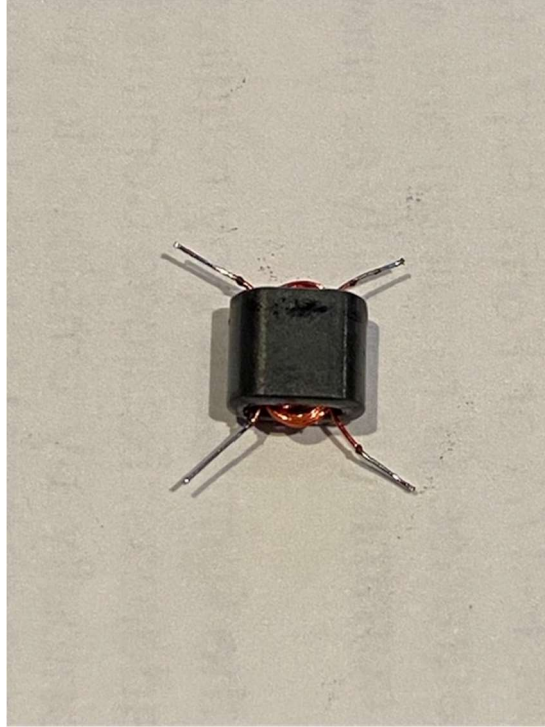


Figure 15. T2 Transformer Ready For Mounting On The PCB.

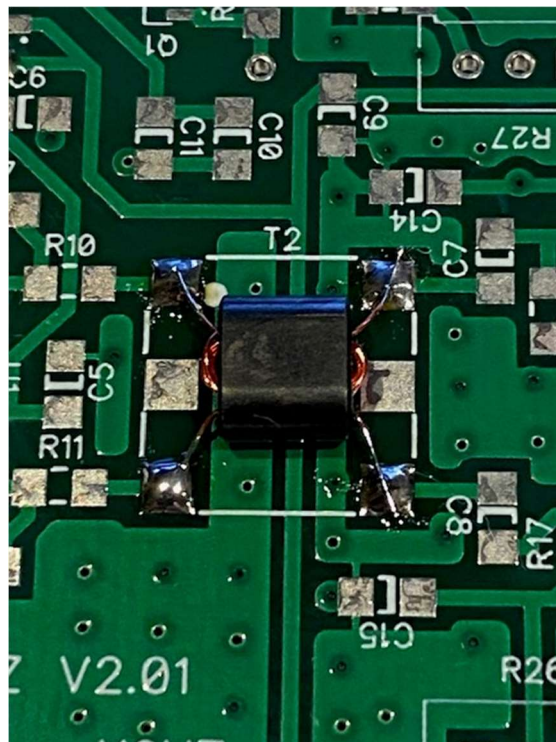


Figure 16. T2 Transformer Soldered In Place On The PCB.



Figure 17. Two Wires Soldered Together To Form The T3 Primary Center Tap.



Figure 18. Legs Placed Into The BN43-3312 Core.



Figure 19. Completed T3 Primary – 1T + 1T.



Figure 20. Completed T3 Secondary – 3T.



Figure 21. T3 Dressed And Ready To Mount On The PCB.

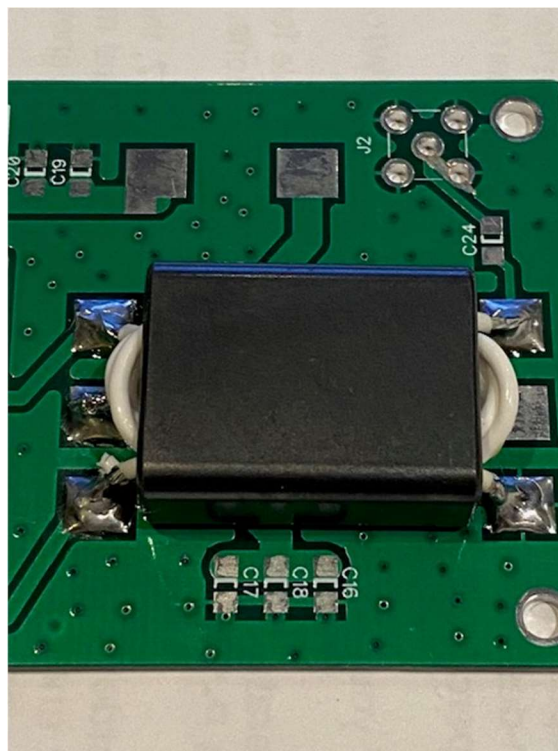


Figure 22. T3 Transformer Soldered In Place On The PCB.

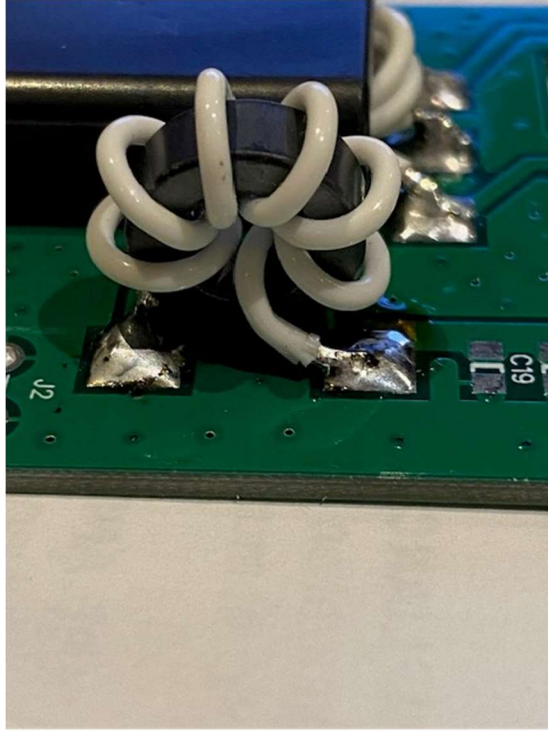


Figure 23. Finished L2 Choke Mounted On The PCB.

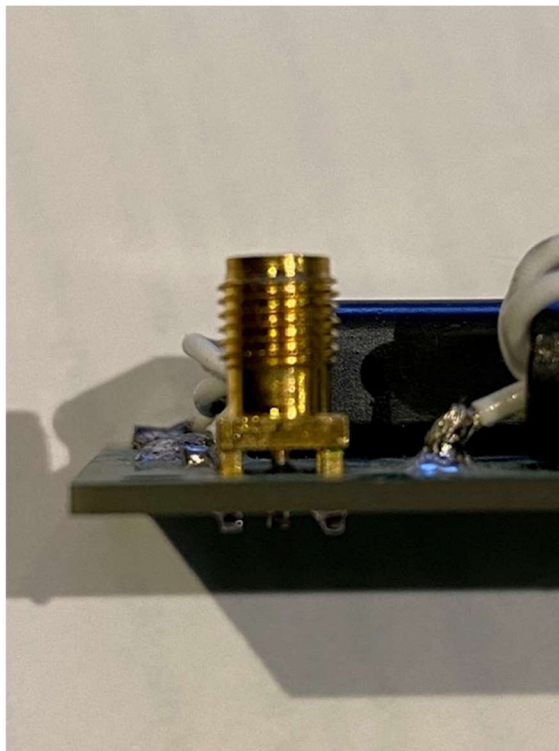


Figure 24. Mounting The SMA Connector.

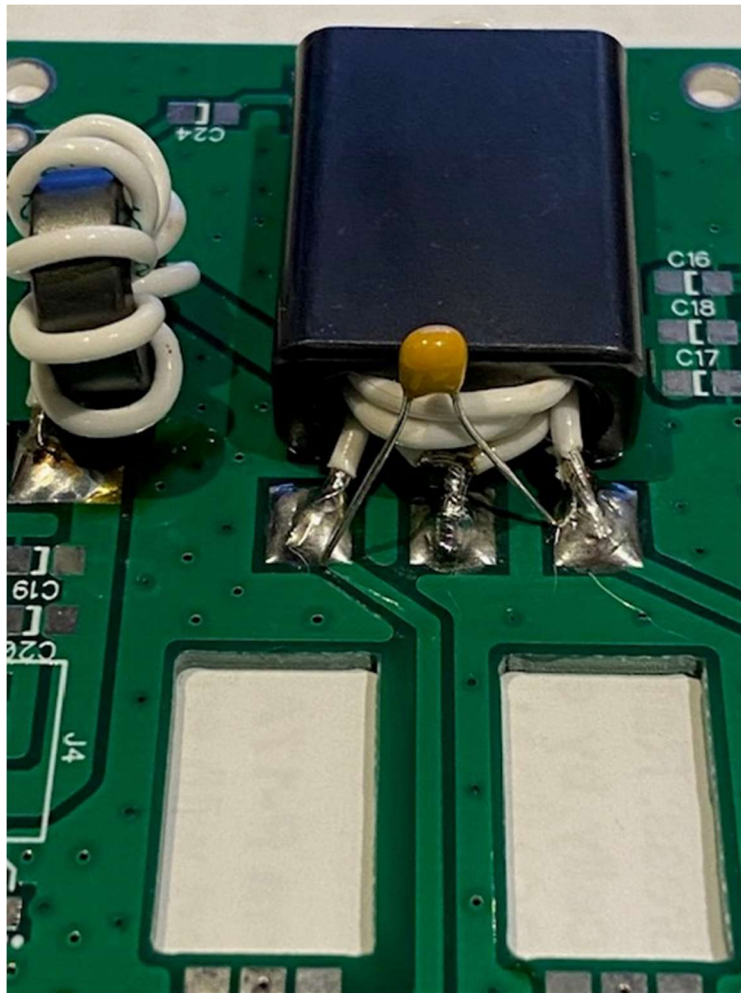


Figure 25. C24 At The Primary Of T3.