

This file contains the updates and notes for the

6-Band RX Bandpass Filter

by David Jordan, K1NQ

Table of Contents

Construction Notes -

Notes from N8RA - Revision 3.0, 10 October 2007 - Reverse D5, Change transistors, Cap sizing, Jumpers, wire size for L1-3, make C18 and C19 parallel, Jumper P3-P7 help, PCB spacers, J3 male on chassis

Inductor construction table updated 29 August 2007

Mechanical parts placement for the TenTec custom enclosure

Updated parts list - updated 10 October 2007

Three modifications from N8RA 1 - LEDs too bright, 2 - Lower SWR when off, 3 - Add AUX RX Antenna - 29 January 2008

PTT Sequencing Circuit – 4 December 2008

Performance Data -

Band plots from K1NQ 7 November 2007

SWR plots from K1NQ

Compiled by KV1J - 4 December 2008

Rev 3.0. **Changes from 2.2 are in bold type.**

10 October 2007

K1NQ, W1UE, KV1J and I have been looking over and building up some portions of the 6BPF boards and have come across some corrections that will need to be done before and as you build the boards. I've volunteered to put out the construction notes.

Essential updates:

1- The silkscreen pattern for D5 (the catch diode near K5) is backwards. The cathode band of this diode needs to go farthest away from the relay, not closest to it as marked. If you don't put this in right then Q4 will burn up when 40M is first energized. (The webpage schematic is not correct in this area either).

2- The transistors listed and sent for Q1-Q6 are the wrong part and should not be installed in the board. They need to be NPN's, not PNP's. PNP's will not work here. Any small signal or switching NPN transistor will do, like 2N3904 or 2N2222. If you do not have any, I suggest Radio Shack part number 276-1617, 15 transistors for \$2.59, enough for 2 boards and a few for your junkbox.

3- Jumper "jump2" needs correction. One side of it should go to the hole marked "jump2" near C56, but do not connect the other end to the hole marked "jump2" under K3. Instead this end of the wire needs to go to one of the pins of relay K8 as shown below. **Use a piece of hookup wire under the board for this, and not RG174.**

Also cut the trace shown.

P4 large relay pads

O O O O

| <-----cut this heavy trace between pins

O--- O O O <-----connect the free end of jumper wire jmp2 to this pad

P5

|
|
o
J2 o

View of K8 solder pads from bottom side of board

4- The holes for L1, L2, and L3 aren't large enough to accept the #16 wire that the toroids are wound with. Drill all the holes out to 1/16", but this will destroy the plating connecting the top pad to the bottom one on the PCB, so make sure to solder the wire on both sides of the board.

Better yet, change to #20 wire to wind these inductors. See the "Inductor construction table (.xls file)" for more details.

5. Capacitors C18 and C19 in the 15M filter section need to be in parallel, not in series as laid out on the PCB. One way to fix this is to solder the two caps together and then bend the leads of one to go from the top hole of the C18 outline to the bottom hole (ground) of the C19 outline.

6. Some of the part designations in the initial documentation on the YCCC website changed on the final PCB. The listing that came with the parts kits is correct. For those that did not get parts kits, refer to the "updated 6bpf parts list" document for a complete listing. Especially note the changes for the 22, 56, 30, and 2.2 pf capacitors. (tnx N1MM)

Helpful information:

A. LED D3: the anode is the long lead and should go to the hole in the square pad. Do not solder this LED into the board. It will be on the front panel with extension leads connecting it to the PCB.

B. Coax jumper on top of board: use a 4" piece of the RG174 to go from "jmp1" located next to J1, over to "JUMP" located near Q1.

C. Bypass capacitors C67-C75 and C80-C86: the parts supplied have too narrow a lead spacing to fit the footprint in the board and need to be spread apart. Use a small needle nose plier to hold the lead when you bend it so as not to introduce small cracks in the seal of the ceramic body. Bend one lead as suggested below. Take care that the horizontal part of the bent lead does not short to any traces on the top of the board that go between the pads. This same technique should also be used for other caps having too close a lead spacing to fit the holes without straining the leads.



D. Capacitor C77 has the opposite problem to that above. Similarly bend one of its leads toward the other to shorten the spacing.


F. Cut lengths for the RG-174 coax.

9 3/4" for the piece going to J1 on the PCB


10 1/4" for the piece going to J2 on the PCB

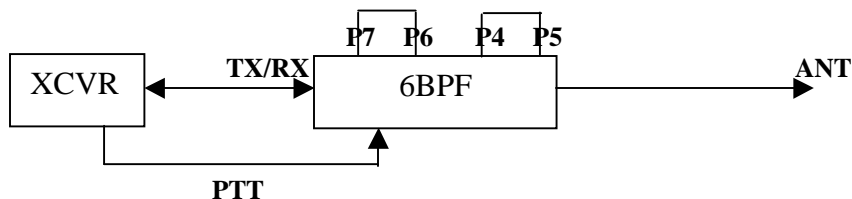G. Wiring of Option Jumpers P3-P7:

For using the filter with a radio that transmits and receives on the same connector (the usual situation), put a jumper between P7 and P6, and another between P4 and P5, and be sure to hook up a PTT signal to the filter. Keep the jumpers at least 1/8" away from other traces on the PCB. (And see K1NQ's warnings about the absolute necessity of using a PTT signal, and its delay requirement.) When you transmit, the TX/RX port of the 6BPF will then be switched directly to its ANT port, bypassing any selected filter section, but you must have proper PTT setup for that to happen.



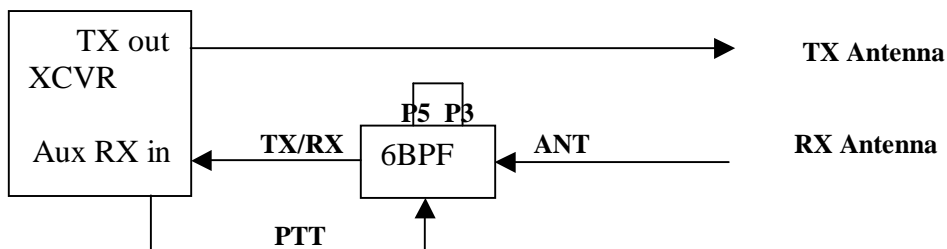For use with a radio's Aux RX input or a separate receiver, put just one jumper between P5 and P3.



This will disconnect the RX antenna and grounds the 6BPF TX/RX port during transmit. Again, see the K1NQ PTT setup warnings.

H. Delay putting in the largest caps until last, as they repeatedly got bent when the board was turned over. They could go in last, after the toroids. (tnx N1MM)

I. For spacers to mount the PCB in the box, use 1/4" high spacers for #6 screws. You can also use 2 dia 5/16" #6 nuts and a #6 flat washer as a spacer.

J. For the band decoder connector (J3) use the MALE on the chassis so that the cable end from the band decoder would not have live conductors exposed when it is not plugged in. The cable end would then be female. (The BOM looks like it has female on the chassis.)

Please let us know of any further comments for this list.

YCCC 6 Band Receive Bandpass Filter

Inductor Winding Table

revision - 29 August 2007

| BAND | REF | CORE | COLOR | WIRE SIZE | WIRE LENGTH | TURNS | NOTES |
|------|-----|--------|--------|-----------|-------------|-------|---|
| 160 | L16 | T50-2 | Red | #24 | 22" | 28 | N8RA needed 31 turns close wound |
| 160 | L17 | T50-2 | Red | #24 | 22" | 28 | N8RA needed 31 turns close wound |
| 160 | L18 | T50-2 | Red | #24 | 22" | 28 | N8RA needed 31 turns close wound |
| 80 | L13 | T50-2 | Red | #22 | 19" | 23 | N8RA used 22 turns spread over 80% of core |
| 80 | L14 | T50-2 | Red | #22 | 19" | 23 | N8RA used 22 turns spread over 80% of core |
| 80 | L15 | T50-2 | Red | #22 | 19" | 23 | N8RA used 22 turns spread over 80% of core |
| 40 | L10 | T50-6 | Yellow | #20 | 16" | 18 | N8RA used 17 turns spread over 80% of core |
| 40 | L11 | T50-6 | Yellow | #20 | 16" | 18 | N8RA used 17 turns spread over 80% of core |
| 40 | L12 | T50-6 | Yellow | #20 | 16" | 18 | N8RA used 17 turns spread over 80% of core |
| 20 | L7 | T50-10 | Grey | #20 | 13" | 15 | N8RA used 13 turns spread over 75% of core |
| 20 | L8 | T50-10 | Grey | #20 | 13" | 15 | N8RA used 13 turns spread over 75% of core |
| 20 | L9 | T50-10 | Grey | #20 | 13" | 15 | N8RA used 13 turns spread over 75% of core |
| 15 | L4 | T50-10 | Grey | #18 | 12" | 10 | N8RA compressed the 10 turns over 60% of core |
| 15 | L5 | T50-10 | Grey | #18 | 12" | 10 | N8RA compressed the 10 turns over 60% of core |
| 15 | L6 | T50-10 | Grey | #18 | 12" | 10 | N8RA compressed the 10 turns over 60% of core |
| 10 | L1 | T50-10 | Grey | #20 | 7" | 8 | N8RA spread the 8 turns over 40% of core |
| 10 | L2 | T50-10 | Grey | #20 | 7" | 8 | N8RA spread the 8 turns over 40% of core |
| 10 | L3 | T50-10 | Grey | #20 | 7" | 8 | N8RA spread the 8 turns over 40% of core |

Note 1: Just putting the wire thru the core with a simple U-turn counts as the first turn.

Note 2 : L1-L3 changed from #16 wire

Note 3: David K1NQ suggests - You should be winding all the cores with the wire spread out to cover 3/4 of the core for best Q.

The core's permeability can vary +/-20% from lot to lot. It is better to start off with the recommended turns and then remove 1 or 2 turns if needed. You can use a MFJ meter to sweep the filter for SWR to center the inductors

Note 4: The W3LPL app notes on K1TTT's website says to tune the filters by squeezing or spreading turns and/or adding or subtracting turns
<http://www.k1ttt.net/technote/w3lplfil.html>


Note 5: N8RA used an Autek RF-1 to look at the SWR thru each filter. The SWR increases very rapidly outside the passband so he adjusts the turns and their initial spacing to achieve low SWR in the band under test.

Final tweaking of spacing is done by listening to that band on the air while switching the filter in and out.

Note 6: W1UE has wound some coils with 1 more turn than nominal and will borrow an MFJ Antenna Analyzer to tune them after they are in the box.

Note 7: The toroids can be wound "CW" or "CCW" on the core.

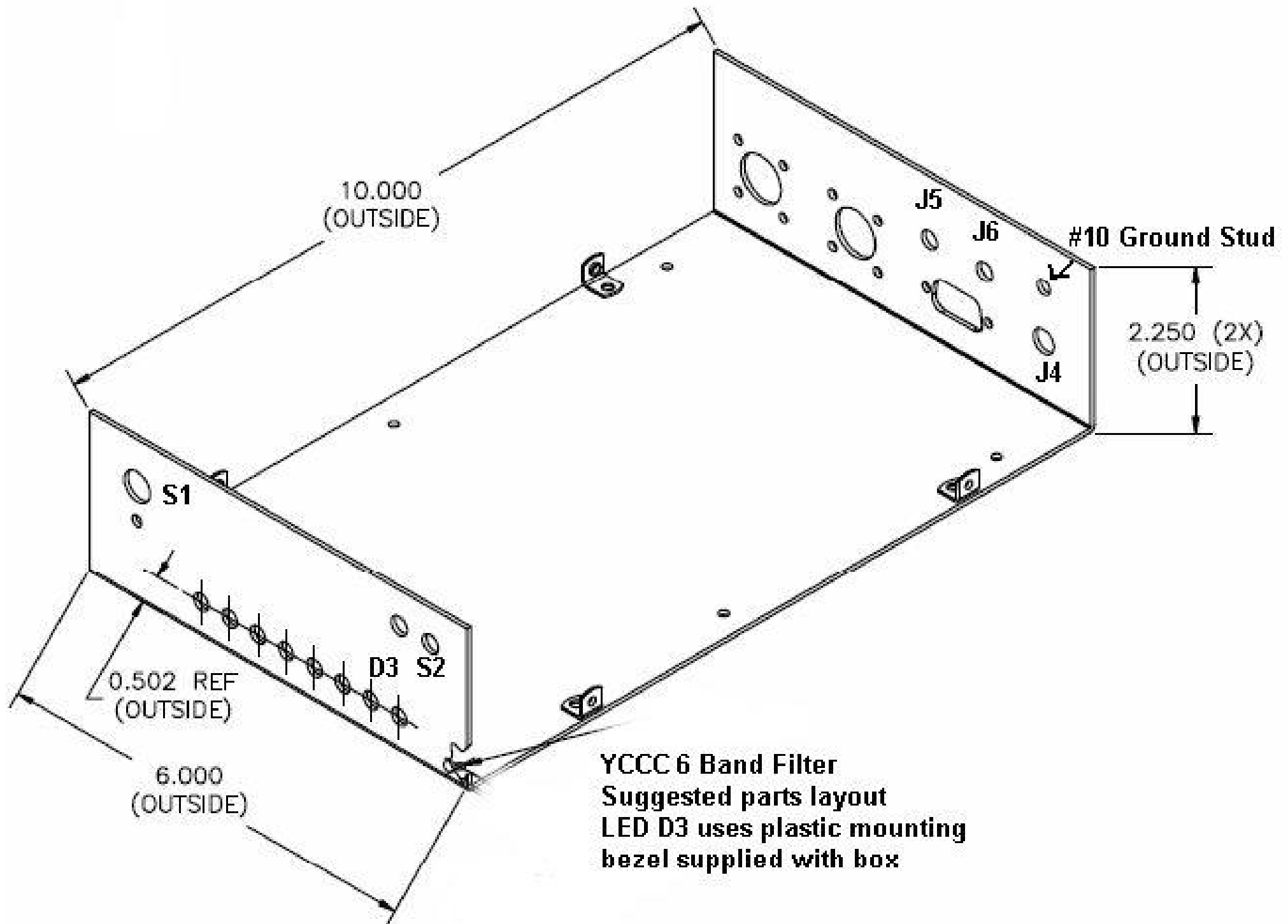One of these ways will match the outline on the PCB, but it makes no difference electrically.



| | | <u>qty</u> | | | | <u>Mouser part no</u> |
|----|-----------------------------|------------|--------|--------------------|-----------|-----------------------|
| 1 | C1,C19 | 2 | 33p | Capacitor | NPO100 | 140-100N5-330J-RC |
| 2 | C2,C3,C4,C22 | 4 | 15p | Capacitor | NPO100 | 140-100N2-150J-RC |
| 3 | C5,C12,C23 | 3 | 10p | Capacitor | NPO100 | 140-100N2-100J-RC |
| 4 | C6,C34 | 2 | 27p | Capacitor | NPO100 | 140-100N5-270J-RC |
| 5 | C7,C45 | 2 | 47p | Capacitor | NPO100 | 140-100N5-470J-RC |
| 6 | C8,C10,C11,C15,C16,C17,C27 | 7 | 56p | Capacitor | NPO100 | 140-100N5-560J-RC |
| 7 | C9,C20,C21,C32,C40,C59 | 6 | 20p | Capacitor | NPO100 | 140-100N2-200J-RC |
| 8 | C13 | 1 | 8.2p | Capacitor | NPO100 | 140-500N2-8R2D-RC |
| 9 | C14,C62,C65 | 3 | 39p | Capacitor | NPO100 | 140-100N5-390J-RC |
| 10 | C18,C28,C44,C49 | 4 | 30p | Capacitor | NPO100 | 140-100N5-300J-RC |
| 11 | C24,C36 | 2 | 2.2p | Capacitor | NPO100 | 140-100N2-2R2D-RC |
| 12 | C25,C30,C35 | 3 | 22p | Capacitor | NPO100 | 140-100N5-220J-RC |
| 13 | C26,C33,C41,C42,C43,C47,C60 | 7 | 150p | Capacitor | SL | 140-102S6-151J-RC |
| 14 | C29 | 1 | 68p | Capacitor | NPO100 | 140-100N5-680J-RC |
| 15 | C31,C37,C46,C48,C53,C54 | 6 | 100p | Capacitor | NPO100 | 140-100N5-101J-RC |
| 16 | C38,C63 | 2 | 180p | Capacitor | SL | 140-102S6-181J-RC |
| 17 | C39,C55 | 2 | 220p | Capacitor | SL | 140-102S6-221J-RC |
| 18 | C50 | 1 | 330p | Capacitor | SL | 140-102S6-331J-RC |
| 19 | C51,C61 | 2 | 470p | Capacitor | SL | 140-102S6-471J-RC |
| 20 | C52,C58 | 2 | 560p | Capacitor | SL | 140-102S6-561J-RC |
| 21 | C56 | 1 | 1000p | Capacitor | SL | 140-102S9-102J-RC |
| 22 | C57,C64 | 2 | 680p | Capacitor | SL | 140-102S6-681J-RC |
| 23 | C66,C78 | 2 | .01u | 200v cap | C322 | 80-C322C103K2R |
| 24 | C67-C75, C80-C86 | 16 | .01U | small cap | C315 | 80-C315C103K5R |
| 25 | C76 | 1 | .001U | small cap | C317 | 140-50Z5-102M-RC |
| 26 | C77 | 1 | .1U | small cap | CK05 | 140-50Q9-104Z-RC |
| 27 | D1,D2,D4-D13 | 12 | 4003 | diode | 1N4003 | 583-1N4003-B |
| 28 | D15,D23 | 2 | 4007 | diode | 1N4007 | 583-1N4007-B |
| 29 | D3 | 1 | 5mm | led orange | | 604-WP7113NC |
| 30 | D14 | 1 | Green | small led RA 5mm | LUMEX | 696-SSF-LXH100MGD |
| 31 | D16 | 1 | YELLOW | small led RA 5mm | LUMEX | 696-SSF-LXH100MYD |
| 32 | D17,D18,D19,D20,D21,D22 | 6 | RED | small led RA 5mm | LUMEX | 696-SSF-LXH100MLID |
| 33 | J1,J2 | 2 | COAXJ | Coax jack | uhf | 601-25-7350 |
| 34 | J3 | 1 | Conn8 | 9 pin male-chassis | 9PIN Dsub | 156-1209 |
| 35 | mate for J3 | 1 | | 9 pin female-cable | 9PIN Dsub | 156-1309 |

| | | | | | | |
|----|-------------------------|-----|---------|----------------------|---------|------------------|
| 36 | hood for J3 mate | 1 | | | | 156-3009-E |
| 37 | J4 | 1 | | 2.5mm power jack | | 163-2325-E |
| 38 | J4 mate | 1 | | 2.5mm power plug | | 1710-2512 |
| 39 | J5 | 1 | | 3.5mm phonejack NC | | 16PJ135 |
| 40 | J5 mate | 1 | | 3.5mm plug | | 17PP103 |
| 41 | J6 | 1 | | phonojack | | 161-0253-EX |
| 42 | K1,K2,K3,K4,K5,K6,K7,K8 | 8 | | OEGDPDT | | 677-OMI-SH-212D |
| 43 | Q1,Q2,Q3,Q4,Q5,Q6 | 6 | 2N3904 | Bipolar | TO92 | |
| 44 | Q7 | 1 | MPSA93 | Bipolar | TO92 | 512-MPSA93 |
| 45 | R1,R2,R3,R4,R5,R6 | 6 | 4.7K | Resistor (USA style) | R25 | 291-4.7K-RC |
| 46 | R10-R17, R7 | 9 | 470 | Resistor (USA style) | R25 | 291-470-RC |
| 47 | R8 | 1 | 3k | Resistor (USA style) | R25 | 291-3K-RC |
| 48 | R9 | 1 | 30K | Resistor (USA style) | R25 | 291-30K-RC |
| 49 | S1 | 1 | SW7 | SP12T switch 1/4"sh | | 105-SR2511F-12RN |
| 50 | knob for S1 | 1 | | KNOB | | 45KN012-GRX |
| 51 | S2 | 1 | SPST | Single pole switch | | 108-0001-EVX |
| 52 | L1,L2,L3 | 3 | #16 8t | T50-10 Inductor | #16 8t | |
| 53 | L4,L5,L6 | 3 | #18 10t | T50-10 Inductor | #18 10t | |
| 54 | L7,L8,L9 | 3 | #20 15t | T50-10 Inductor | #20 15t | |
| 55 | L10,L11,L12 | 3 | #20 18t | T50-6 Inductor | #20 18t | |
| 56 | L13,L14,L15 | 3 | #22 23t | T50-2 Inductor | #22 23t | |
| 57 | L16,L17,L18 | 3 | #24 28t | T50-2 Inductor | #24 28t | |
| 58 | coax | 2 | feet | RG316 or RG174 | | |
| 59 | | 8 | feet | #24 MAGNET WIRE | | |
| 60 | | 6 | feet | #22 MAGNET WIRE | | |
| 61 | | 12 | feet | #20 MAGNET WIRE | | |
| 62 | | 3 | feet | #18 MAGNET WIRE | | |
| 63 | | 2.5 | feet | #16 MAGNET WIRE | | |

3 Mods for the 6BPF's de N8RA

The first try to use these filters was the past WWDXCW. KD1EU and I set up two radios here, each equipped with a 6BPF. The filtering performance was great, but that first use did suggest a few things that could be enhanced.


Mod 1: Front Panel LEDs Too Bright

The 6 LED's indicating the band setting of the 6BPF were too bright when the filter was sitting on top of the radio. The fix was to increase their series resistance by adding a 4.7K ohm resistor in series with each existing 490 ohm one. An easy way to do this is to heat the bottom of one of the solder pads of the existing resistor while gently pulling out the corresponding lead on the top of the board. Then trim one lead of the new 4.7K resistor to 1/8", and while heating the same bottom pad again, insert this short end into the hole. The free ends of the two resistors can then be joined together above the PCB.

Mod 2: Lower SWR through the filter when it is turned off

On the second day of the WWDX contest, I started to notice an intermittent in the switching of the T/R bypass operation of the 6BPF. When coming back to receive, sometimes the band would appear dead, but a quick cycling of the 6BPF bypass relays with the front panel power on/off switch or the ptt would bring it back. I think (without any proof) that the relay contacts were damaged by hot switching them when I used the "TUNE" button on the Orion. This TUNE is independent of the delay I had set in the N1MM logger, and RF comes out of the radio very soon after its PTT-OUT switches. So I now have a flaky 6BPF; what to do? Well I could replace the relays but that looks like major surgery. Another desire has been to change the bypass switching arrangement to lower the swr thru the filter when it is powered off. Taking care of both of these needs has turned out to be easy by adding another relay. I used an open frame one with 10A contacts and a 12V coil. If I ever damage the contacts again, I can now clean them. N1MM will say I made lemonade.

This schematic shows how to do it:

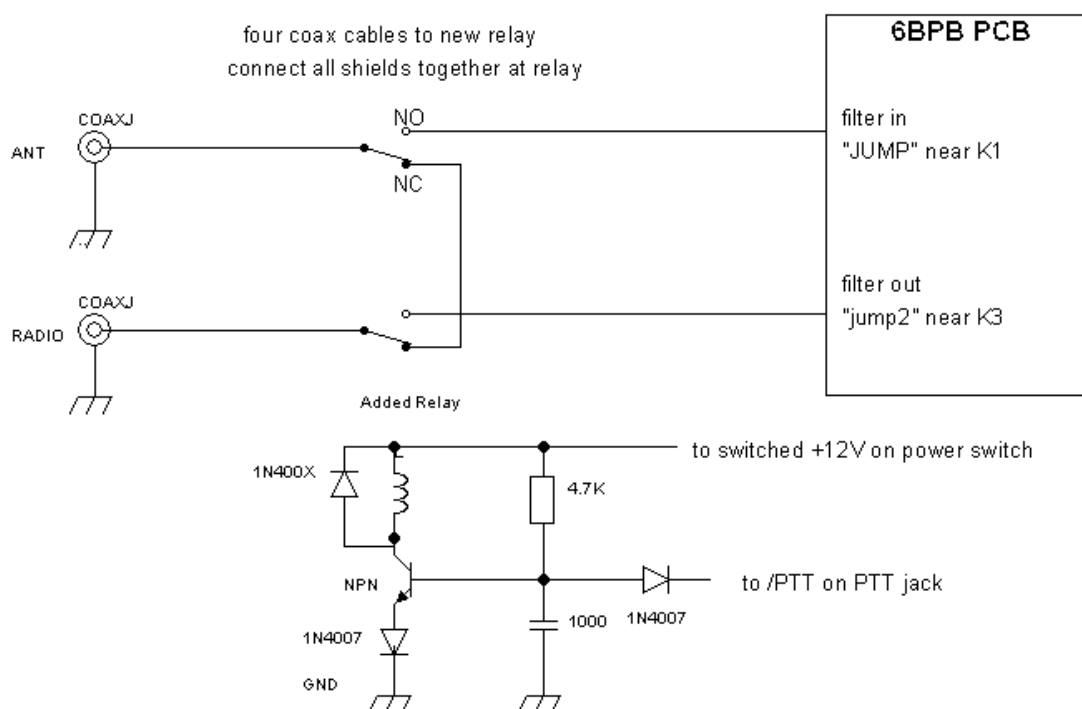


With this arrangement, when the power is off, or when PTT is asserted, the relay is de-energized and bypasses the filter. Because of the short connections, the swr thru the filter is now less than 1.3 to 1 from 160-10M when it is off. When the power is turned on, the relay is energized, and the filter will be “in-line”.

I epoxied a dpdt relay to the center of the PCB and routed the existing coax lines from the antenna and radio back panel SO239's so they now go to the poles of the new relay. Add a wire across the normally closed relay contacts. When the relay is not energized the filter PCB is completely out of the line.

Then wire the input and the output of the filter to the appropriate normally open contacts on the relay. Specifically, route a coax from the filter input, labeled “JUMP” near K1, and one from the filter output labeled “jump2” between K7 and K3 to the relay's NO antenna and radio contacts. Solder the coax shields of these 4 coaxes together at the relay.

To control the relay, add a transistor switch for the coil and tie it into the existing PTT wiring in the 6BPF. I built this circuitry right on the relay coil contacts. The connection to common was made with a bare wire going down to the PCB and soldered to the topside ground foil after scraping away a bit of the solder-mask.

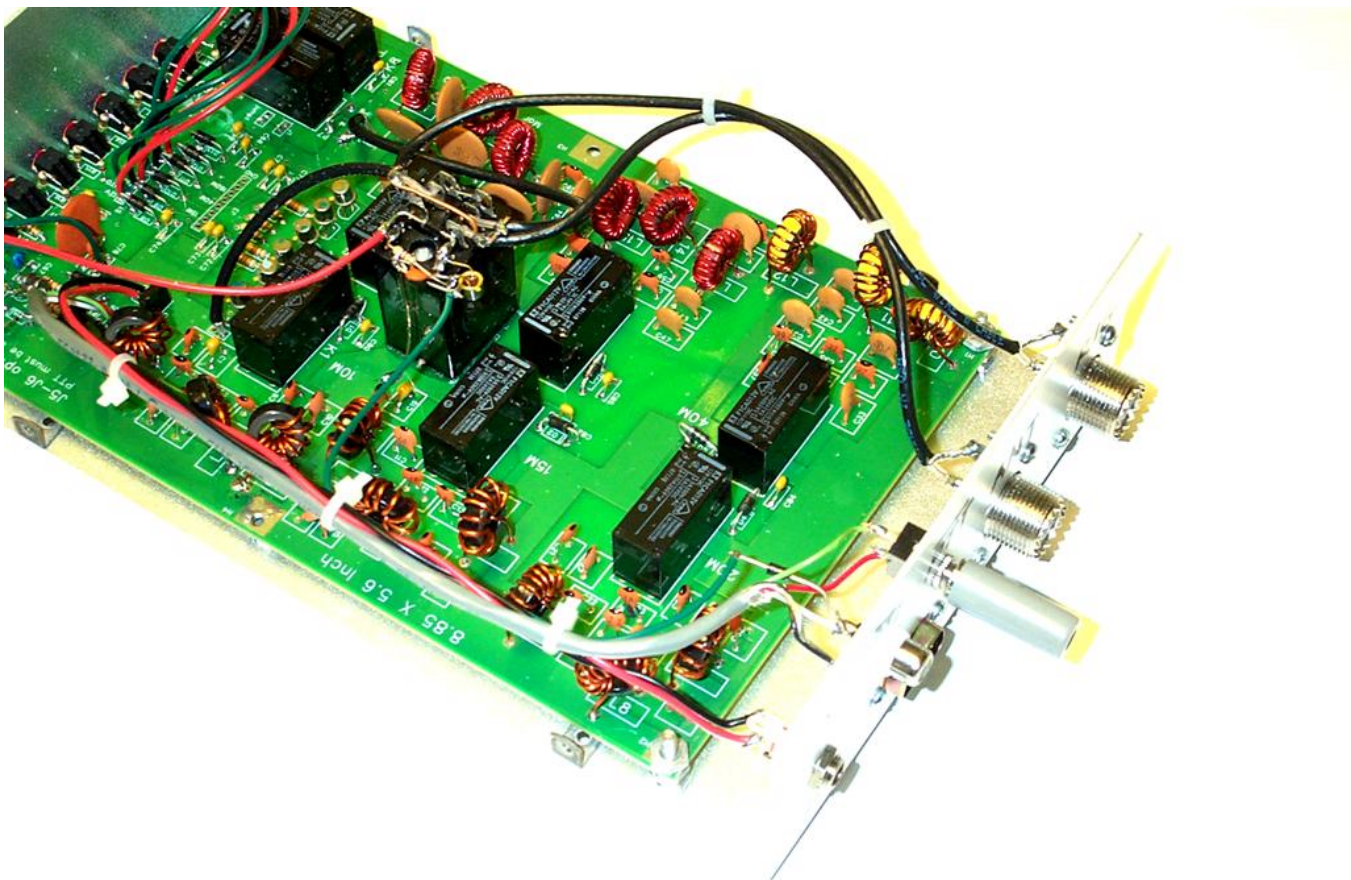
Finally, cut the control line PCB trace to the former T/R relays K3 and K8 since they are no longer used. I cut this trace on the top of board where it runs by R12 and R13.




The photo above shows where I put the relay.

Mod 3) Adding an Aux Receive Antenna Input

The 6BPF works great when you receive and transmit on the same antenna. Sometimes you may want to use it with an aux receive antenna, like a beverage, to benefit from the filtering and receiver front end protection. This is easy. Add another small coaxial connector (like a phono) to the back panel with a coax going from it to a new SPDT switch added to the front panel. Cut the coax going to the filter input labeled “jump” and stretch it, or use two longer pieces that go to the new spdt switch. Wire the SPDT switch to allow selection of either the transmit or the aux antenna feeding the input of the filter. This is also a good way to add an aux antenna input to a radio that does not have one.

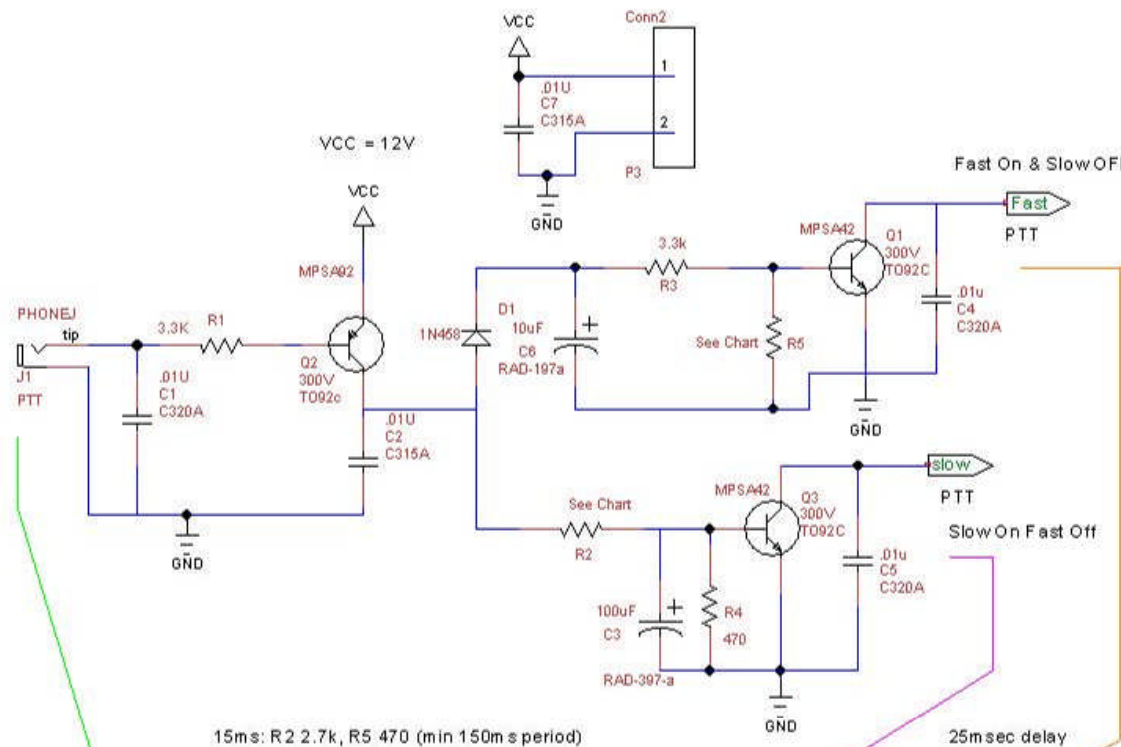

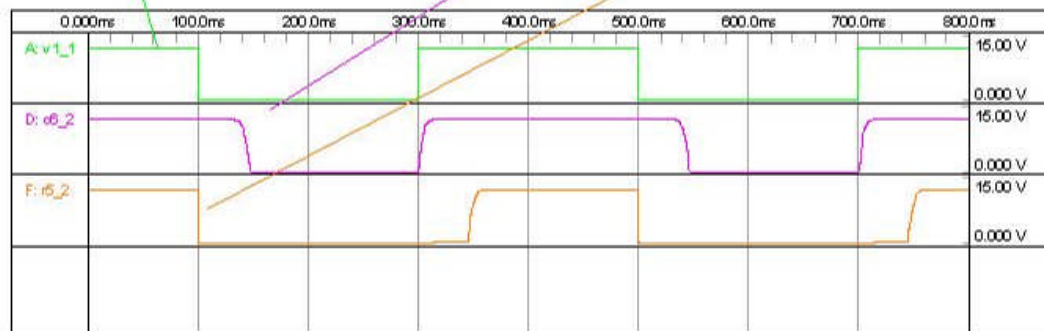15ms: R2 2.7k, R5 470 (min 150ms period)
 20ms: R2 3.3k, R5 560 (min 150ms period)
 25ms: R2 3.9k, R5 680 (min 150ms period)
 35ms: R2 4.7k, R5 1k (min 200ms period)
 50ms: R2 5.6k, R5 1.5k (min 300ms period)
 Minimum delay values (assume 50% duty cycle):



| | | |
|-----------------------------|----------------------------------|---------------|
| Title PTT FAST/SLOW CIRCUIT | | |
| Author K1NQ/KK1L | | |
| File | C:\Program Files\TinyCAD\PTT.dsn | |
| Revision 1.1 | Date Dec 4, 2008 | Sheets 1 of 1 |


KING 6Band RXA/KR tune

6 Nov 2007 13:26:57

CH1 S21/M log MAG

10 dB/ REF 0 dB

4: -44.959 dB

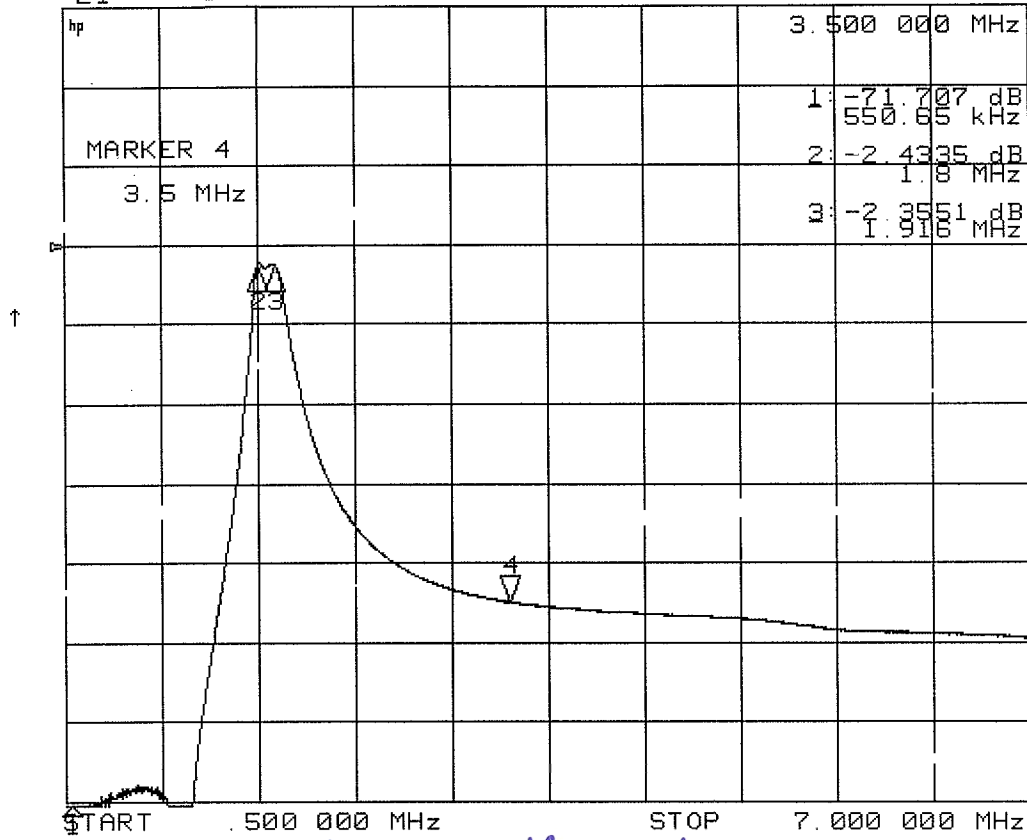

N8RA Inductors all Bands
KING Rev 3/07 Rev B


6 Nov 2007 13:29:18

CH1 S₂₁/M log MAG

10 dB/

REF 0 dB

4: -44.015 dB

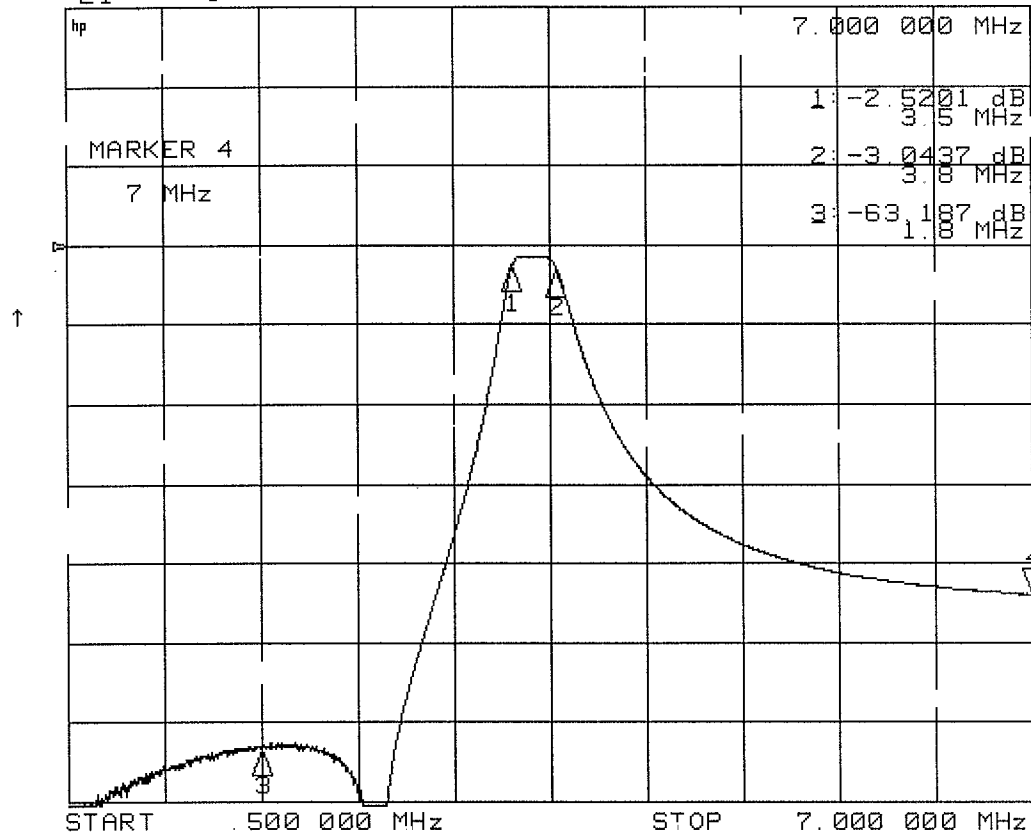


6 Nov 2007 13:32:36

CH1 S₂₁/M log MAG

10 dB/

REF 0 dB

4: -41.81 dB

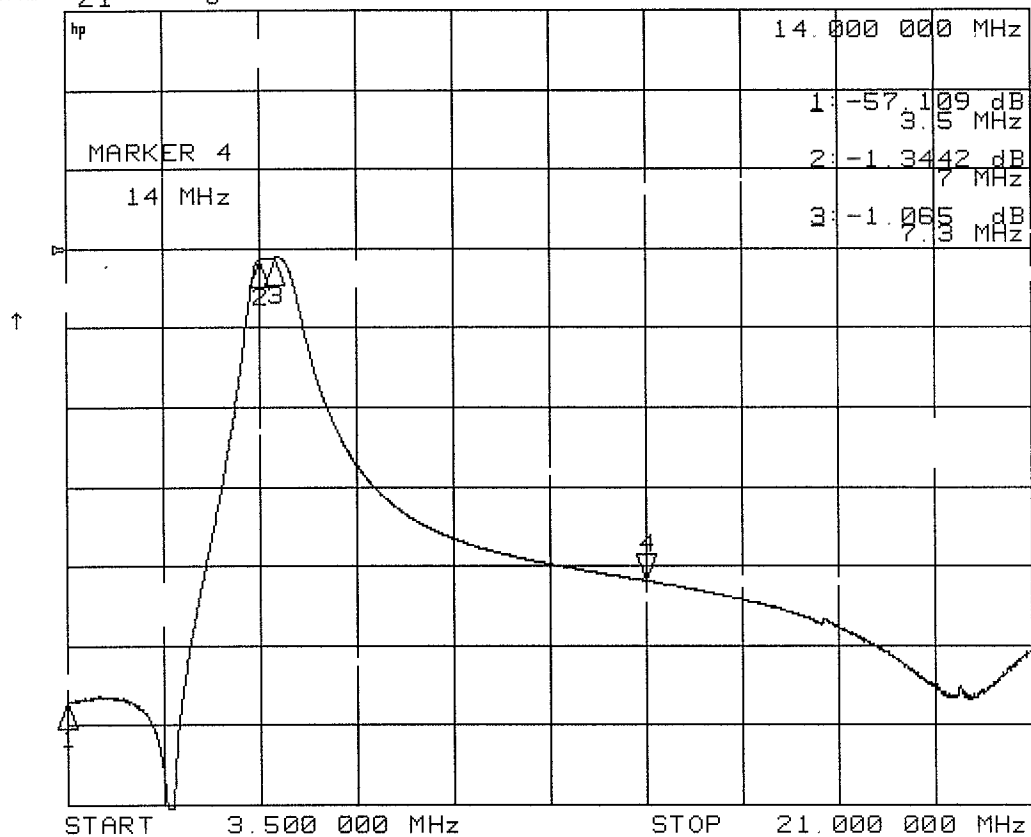


6 Nov 2007 13:34:37

CH1 S₂₁/M log MAG

10 dB/

REF 0 dB

4: -33.207 dB

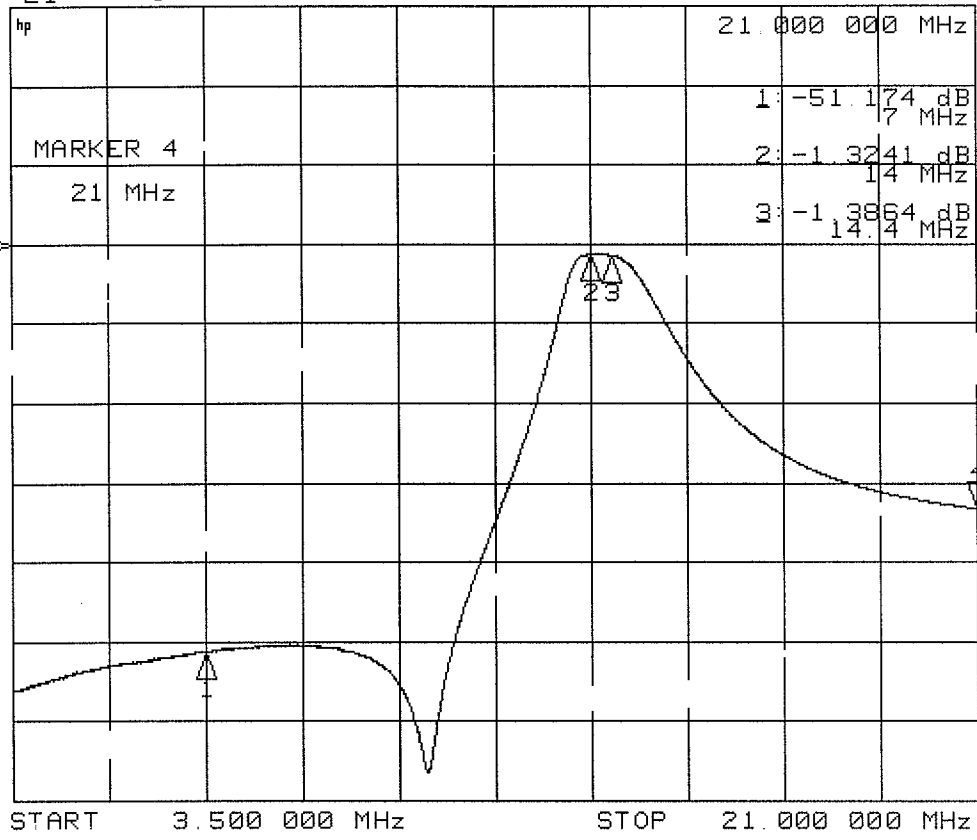


6 Nov 2007 13:38:41

CH1 S₂₁/M log MAG

10 dB/

REF 0 dB

4: -27.468 dB

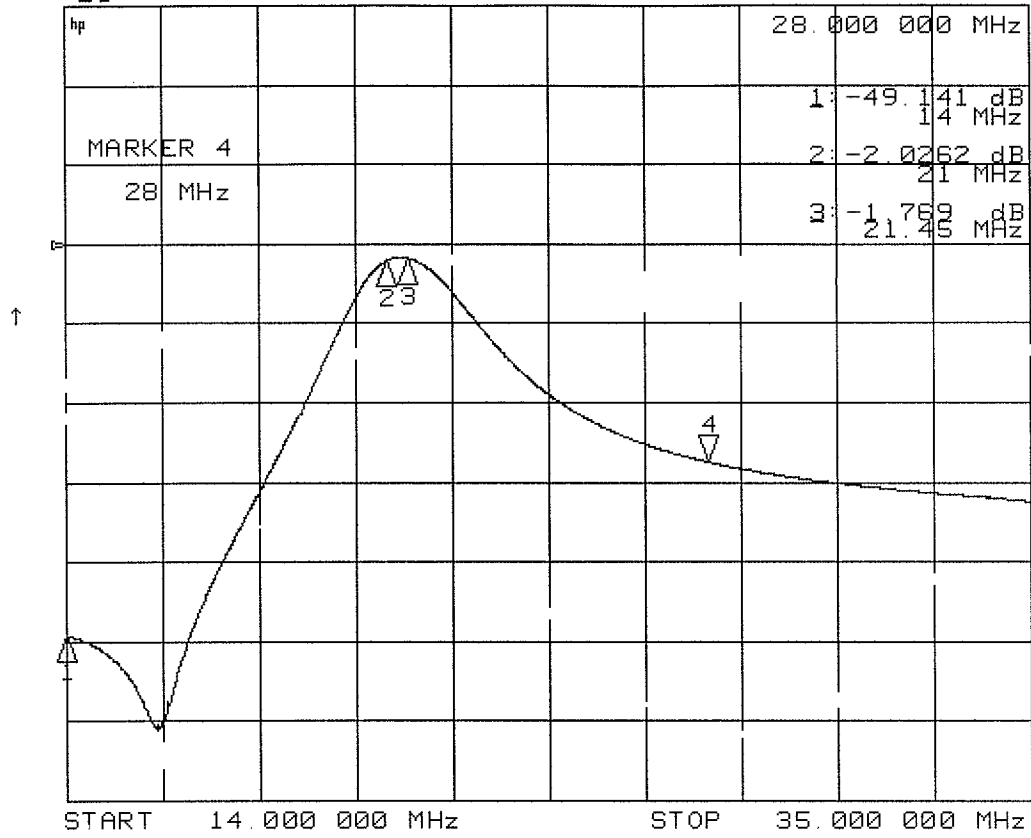


6 Nov 2007 13:39:58


CH1 S₂₁/M log MAG

10 dB/

REF 0 dB

4: -1.5597 dB

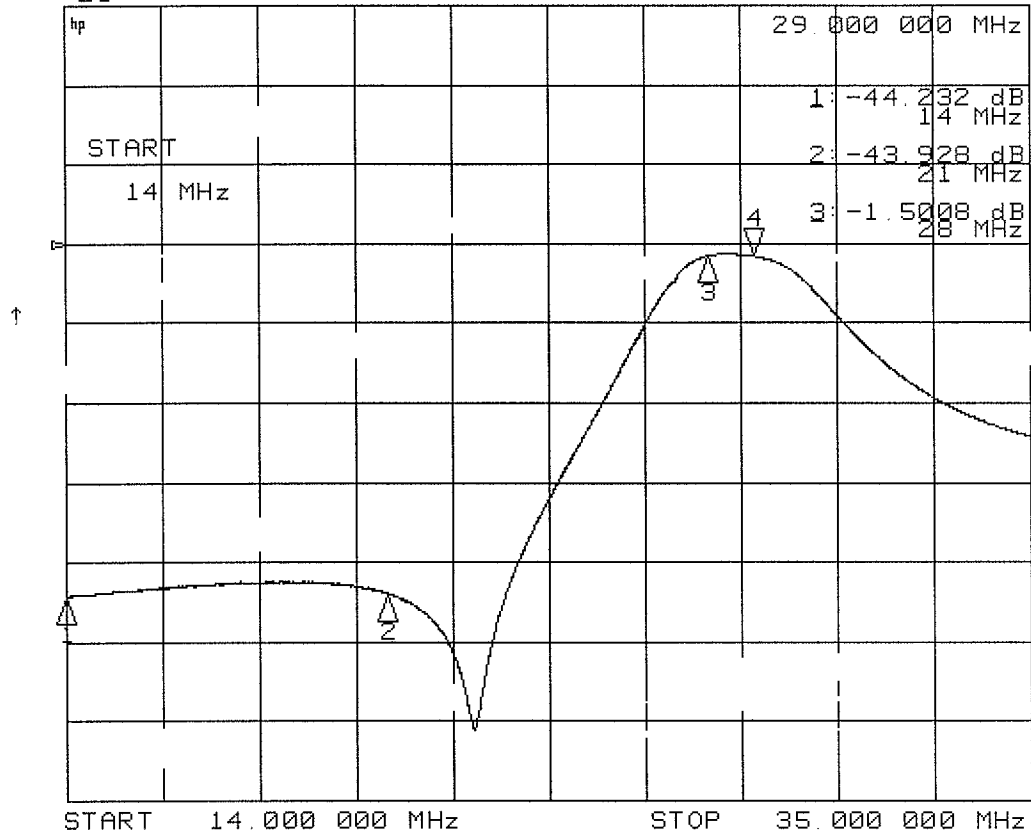


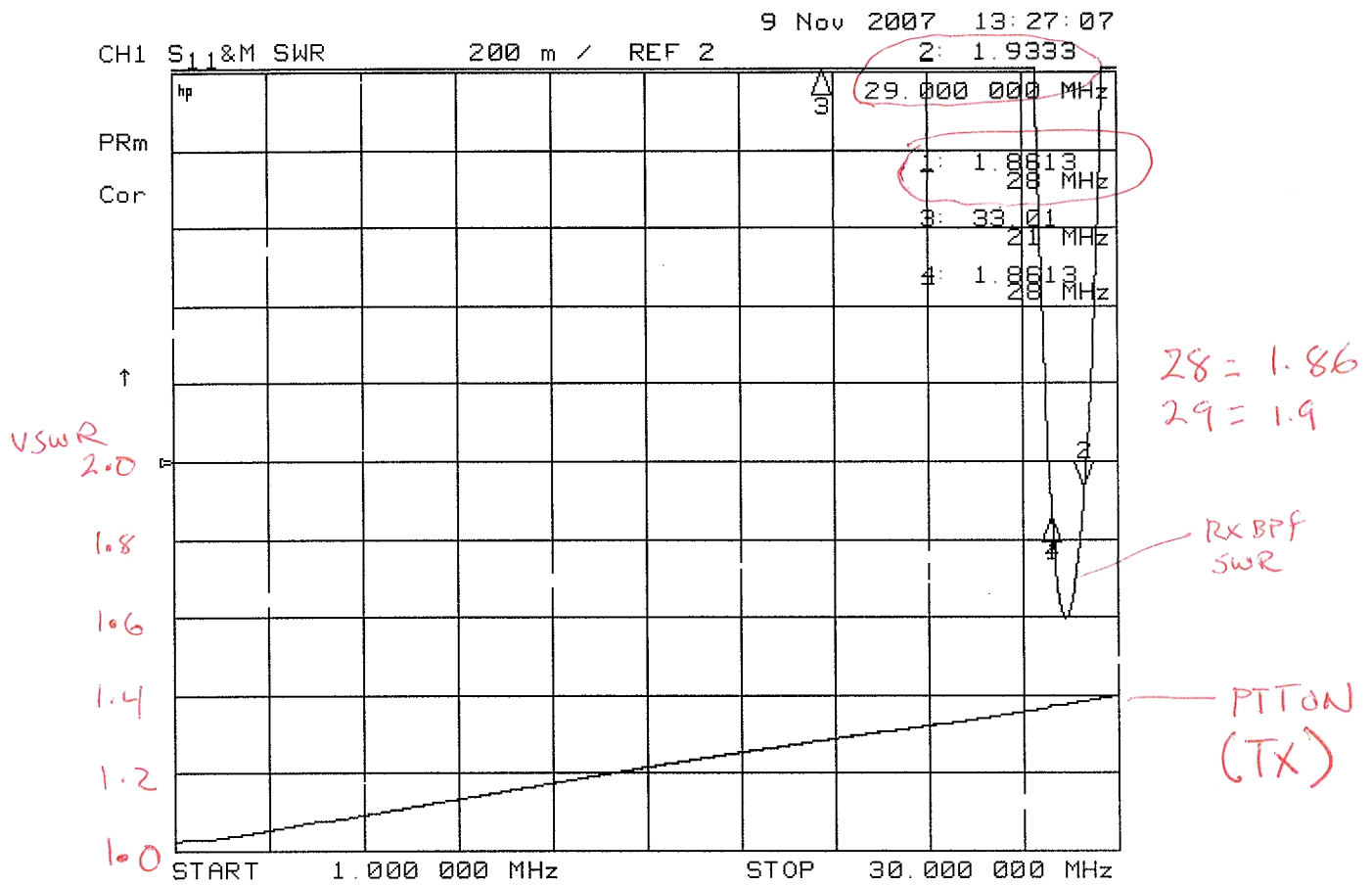

PTT = TX SWR max = 1.4 @ 30 mhz


Note W/o power SWR is $\geq 2:1$ at 28 mhz

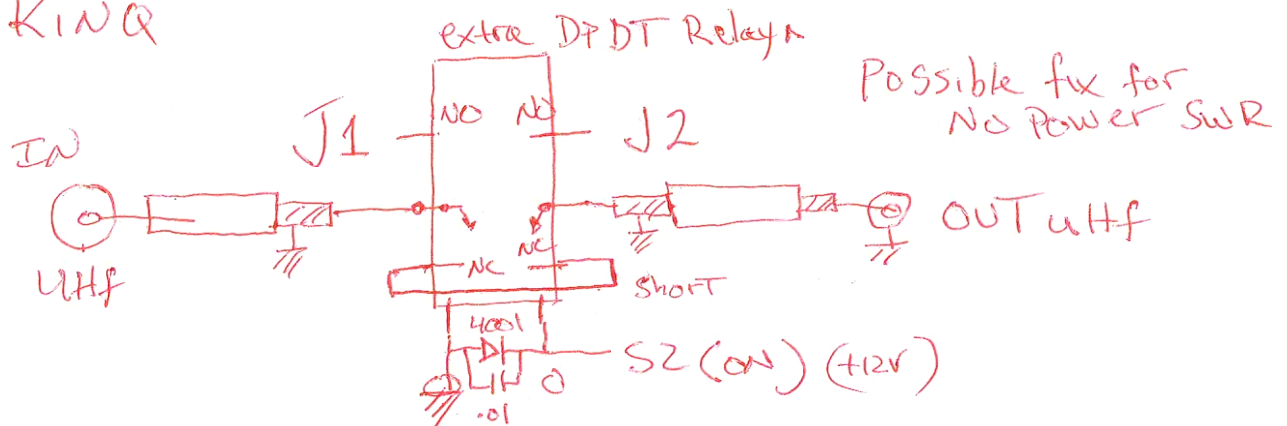Unit was not designed for no power mode
KING



CH1 S11 & M SWR 200 m / REF 2

4: 2.1713

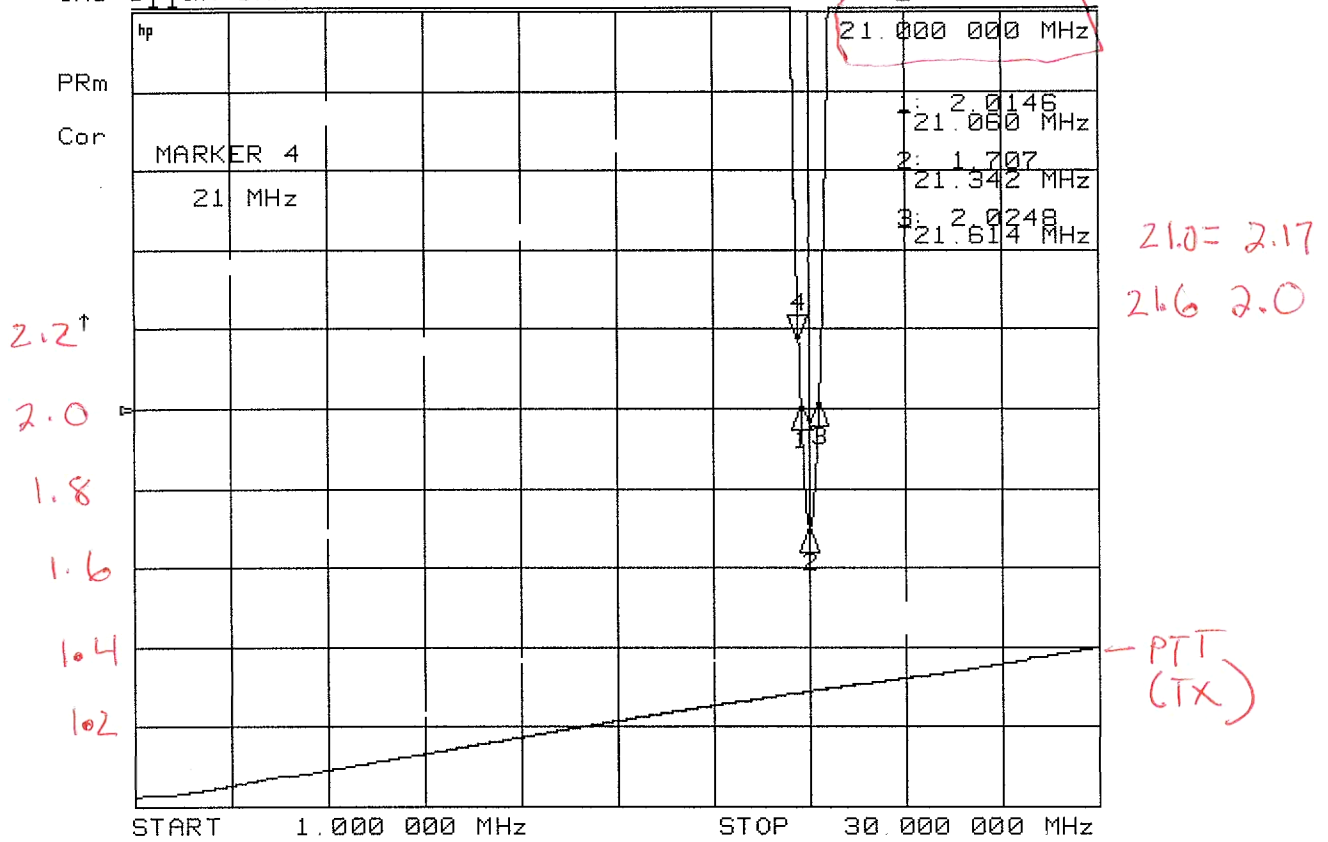


9 Nov 2007 13:29:13

CH1 S11 & M SWR

200 m / REF 2

4: 1.9845

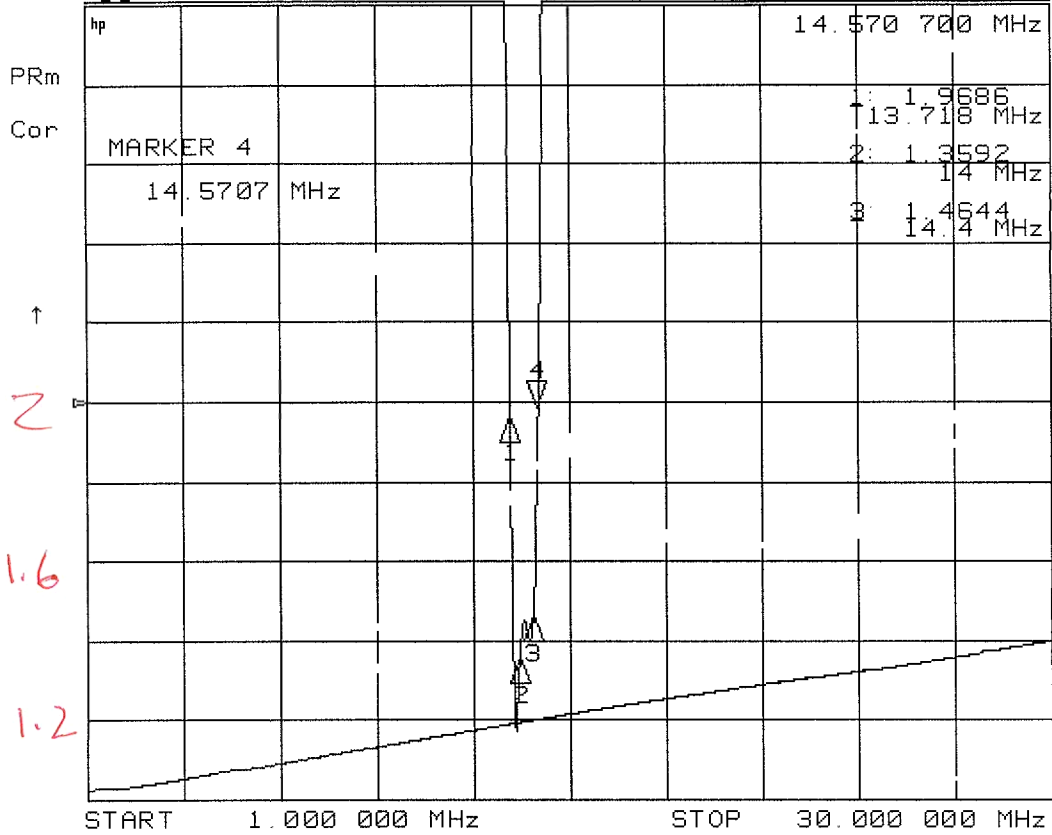


9 Nov 2007 13:31:49

CH1 S₁₁ & M SWR

200 m / REF 2

4: 1.9818

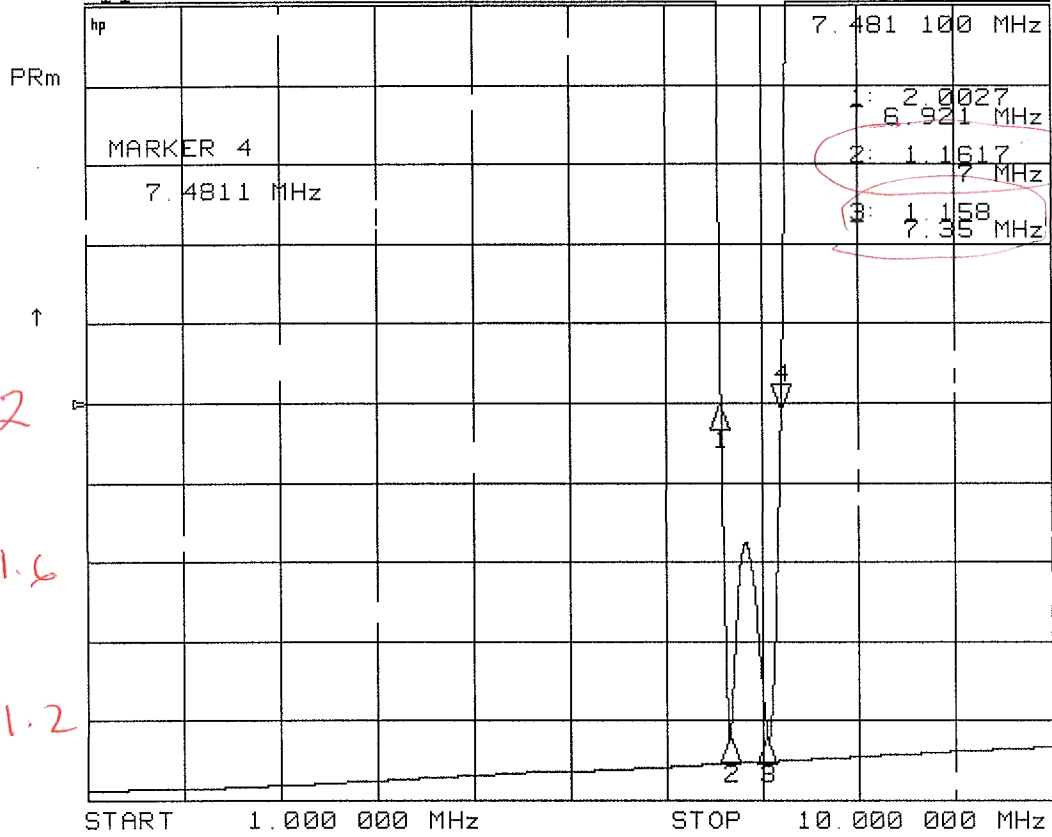

9 Nov 2007 13:32:57

CH1 S11&M SWR

200 m / REF 2

4: 2.9257

30

PRm

MARKER 4

3.8 MHz

3.800 000 MHz

1: 2.2635

3.5 MHz

2: 1.9756

3.506 MHz

3: 1.9672

3.772 MHz

3.5 2.26

3.77=2.0

3.8 = 2.9

2.2 ↑

2

1.6

1.2

START

1.000 000 MHz

STOP


10.000 000 MHz

9 Nov 2007 13:35:25

CH1 S₁₁/M SWR

500 m / REF 3

4: 2.9784

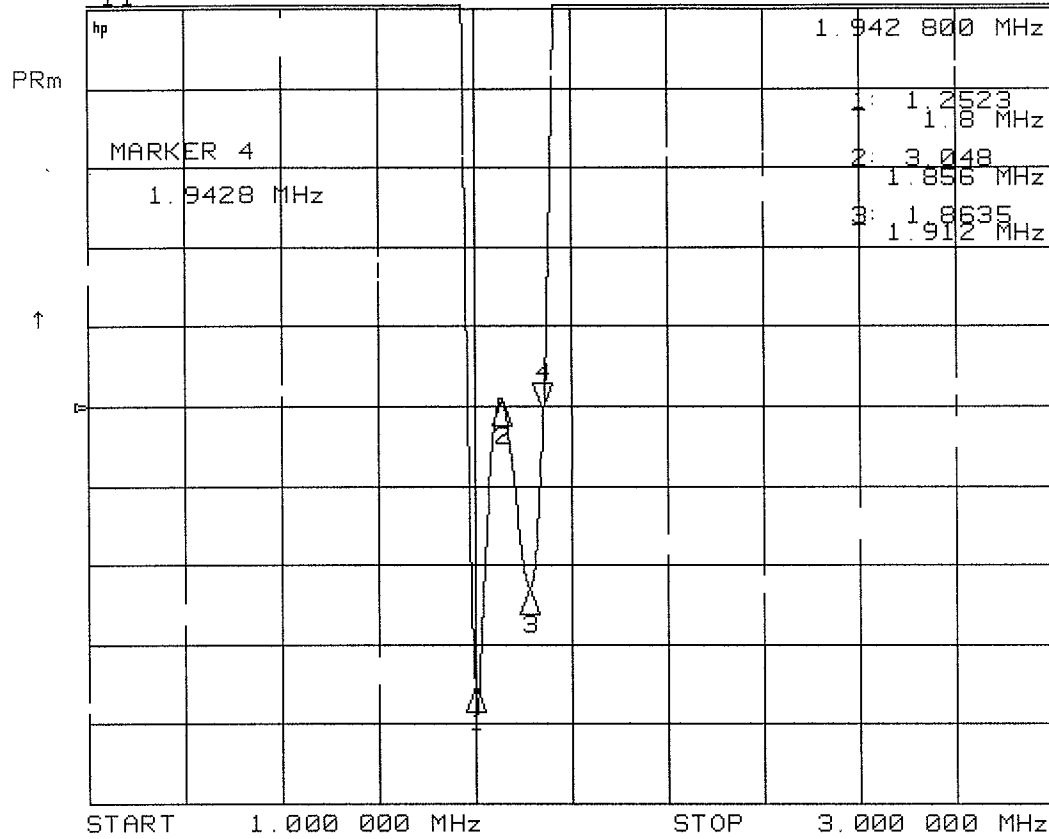

1.8 1.25

1.856 3.0

1.912 1.86

1.942 3.0